

# Arithmetic Circuits: Subtractors, Multipliers, ALU


Becker/Molitor, Chapter 9.2+9.3

Harris/Harris, Chapter 5.2

Jan Reineke

Universität des Saarlandes

# Roadmap: Computer architecture

 

1. Combinatorial circuits: Boolean Algebra/Functions/Expressions/Synthesis
2. Number representations
3. Arithmetic Circuits: Addition, **Multiplication, Division, ALU**
4. Sequential circuits: Flip-Flops, Registers, SRAM, Moore and Mealy automata
5. Verilog
6. Instruction Set Architecture
7. Microarchitecture
8. Performance: RISC vs. CISC, Pipelining, Memory Hierarchy

# Subtraction

As we have  $-[b] = [\bar{b}] + 1$  the difference  $[a] - [b]$  is equal to the sum  $[a] + [\bar{b}] + 1$ .

- Derive subtractor circuit from adder circuit
- combined adder/subtractor

# Reminder: Two's complement

## Lemma:

Let  $d$  be a fixed-point number and  $\bar{d}$  the number obtained by flipping all bits ( $0 \rightarrow 1$ ,  $1 \rightarrow 0$ ) in  $d$ .

Then:  $[\bar{d}]_2 + 1 = -[d]_2$ .

Example:  $n = 2$ ,  $k = 0$ :

$d$	000	001	010	011	100	101	110	111
$[d]_2$	0	1	2	3	-4	-3	-2	-1

# Example: Subtraction


$$[a]_2 = [0110]_2 = 6_{10}$$

$$[b]_2 = [0111]_2 = 7_{10}$$


$$[\bar{b}]_2 = [1000]_2 = -8_{10}$$

0	1	1	0
1	0	0	0
			1
<hr/>			
1	1	1	1
$= (-1)_{10}$			

# Schematic of a subtractor

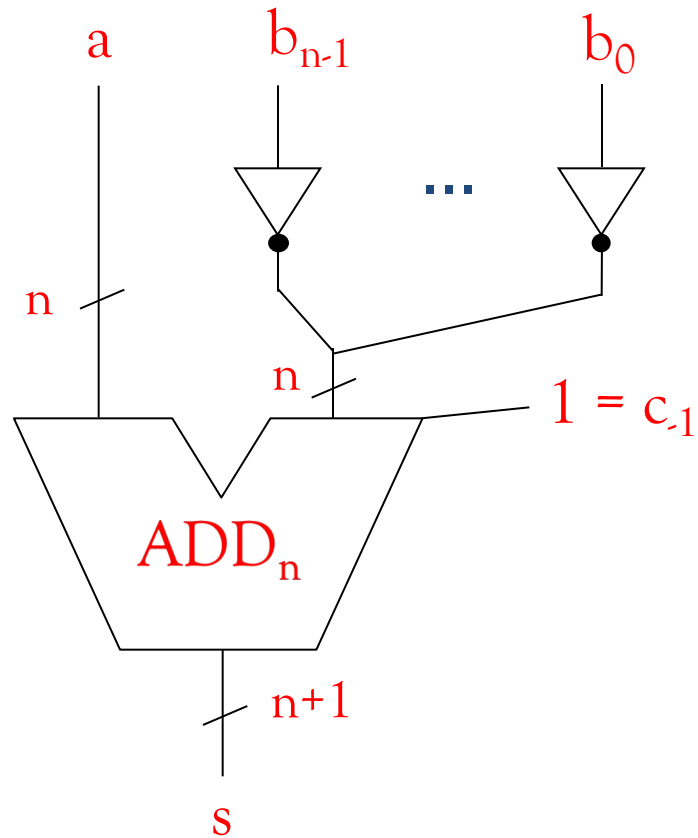
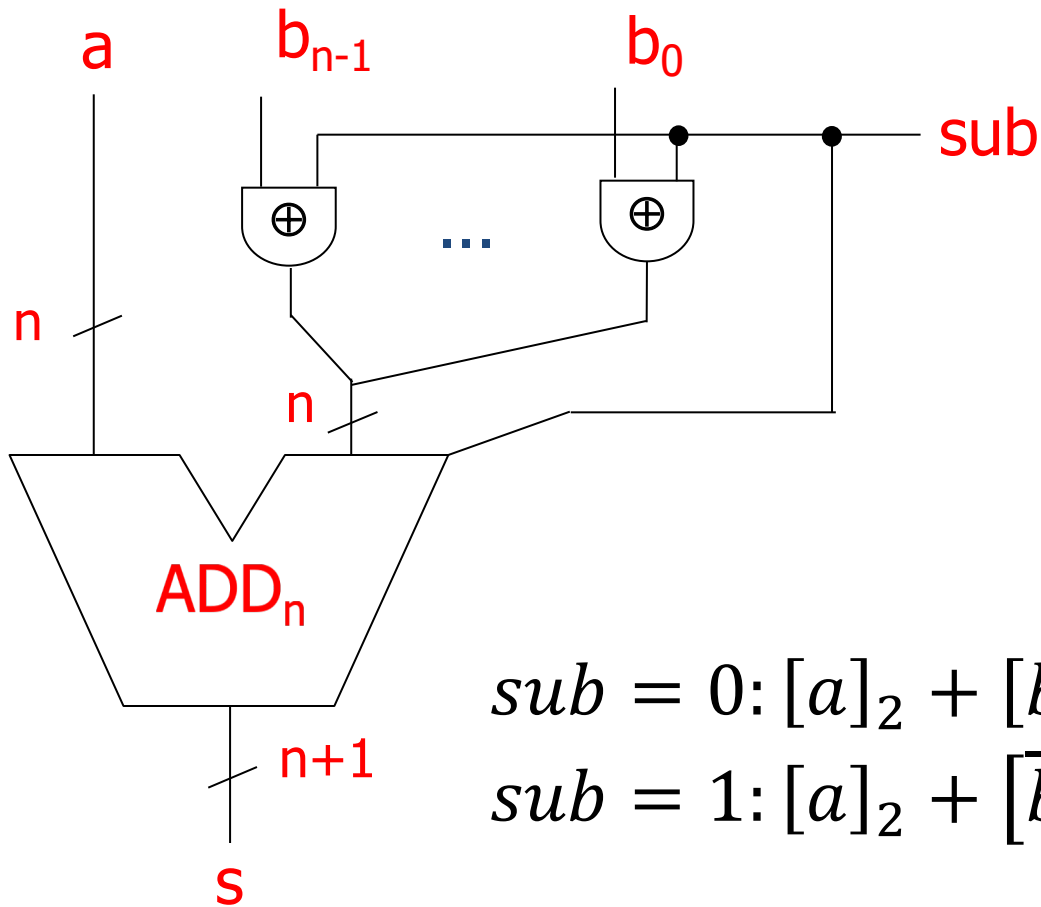
# Schematic of a combined adder/subtractor



$$b_i \oplus 0 = b_i$$

$$b_i \oplus 1 = \bar{b}_i$$

$$sub = 0: [a]_2 + [b]_2 + 0$$

$$sub = 1: [a]_2 + [\bar{b}]_2 + 1 = [a]_2 - [b]_2$$

# Multiplier

Wanted: Circuit for the **multiplication** of two binary numbers  $\langle a_{n-1}, \dots, a_0 \rangle$ ,  $\langle b_{n-1}, \dots, b_0 \rangle$ .

Example:

$$(110) \cdot (101) \\ = 6_{10} \cdot 5_{10}$$

$$\begin{array}{r} \phantom{110} \phantom{00} 1 \phantom{00} 1 \phantom{00} 0 \\ \phantom{110} 0 \phantom{00} 0 \phantom{00} 0 \\ 1 \phantom{00} 1 \phantom{00} 0 \\ \hline 1 \phantom{00} 1 \phantom{00} 1 \phantom{00} 1 \phantom{00} 0 \end{array}$$

$$= 30_{10}$$



# Outputs of a multiplier

How many bits are required for the result?

$$\langle a \rangle \cdot \langle b \rangle \leq$$

$$\left(2^n - 1\right) \cdot \left(2^n - 1\right) = 2^{2n} - 2^{n+1} + 1 \leq 2^{2n} - 1$$

*Thus: **2n bits** are sufficient to represent the product of two n-bit binary numbers.*

# Multiplier

*Definition:* An **n-bit multiplier** is a circuit that computes the following function:

$$\text{mul}_n: \mathbf{B}^{2n} \rightarrow \mathbf{B}^{2n} \text{ with}$$

$$\text{mul}_n(a_{n-1}, \dots, a_0, b_{n-1}, \dots, b_0) = (p_{2n-1}, \dots, p_0) \text{ with}$$


$$\langle p_{2n-1}, \dots, p_0 \rangle = \langle a \rangle \cdot \langle b \rangle$$

$$\langle a \rangle \cdot \langle b \rangle \stackrel{\text{Def. } \langle \cdot \rangle}{=} \langle a \rangle \cdot \sum_{i=0}^{n-1} b_i \cdot 2^i = \sum_{i=0}^{n-1} \underbrace{\langle a \rangle \cdot b_i \cdot 2^i}_{\text{partial product}}$$
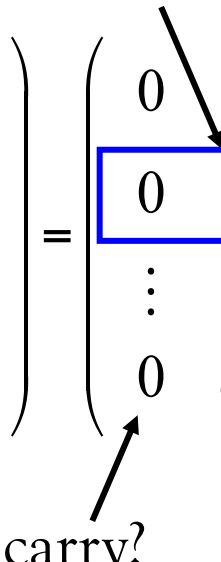
# The multiplication matrix

$n$  partial products, each with  $2n$  bits

$$\begin{pmatrix} pp_0 \\ pp_1 \\ \vdots \\ pp_{n-1} \end{pmatrix} = \begin{pmatrix} 0 & 0 & \dots & 0 & 0 & a_{n-1}b_0 & a_{n-2}b_0 & \dots & a_1b_0 & a_0b_0 \\ 0 & 0 & \dots & 0 & a_{n-1}b_1 & a_{n-2}b_1 & a_{n-3}b_1 & \dots & a_0b_1 & 0 \\ \vdots & \vdots & \vdots & \vdots & \vdots & \vdots & \vdots & \vdots & \vdots & \vdots \\ 0 & a_{n-1}b_{n-1} & \dots & a_2b_{n-1} & a_1b_{n-1} & a_0b_{n-1} & 0 & \dots & 0 & 0 \end{pmatrix}$$



Implementation of the mult. matrix?

→ with  $n^2$  AND gates

(and  $n^2$  constants 0).

# Fast addition of partial products

*Goal:* Fast addition of  **$n$  partial products** of length  $2n$ .

First approach:

Use carry-lookahead adders (CLAs).

Cost:  $O(n^2)$

*Depth:*

- $O(n \cdot \log n)$  if partial products are summed up one by one linearly
- $O(\log^2 n)$  ( $= O((\log n)^2)$ ) for tree-shaped summation of partial products

*Brainstorming:*

Addition of partial products:

Can we do better than adding up the partial products in  $O(\log^2 n)$ ?

# Fast addition of **n partial products**


Use **carry-save adders**.

Reduction of three input values  $u$ ,  $v$ ,  $w$  into two output values  $s$ ,  $c$  s.t.  $\langle u \rangle + \langle v \rangle + \langle w \rangle = \langle s \rangle + \langle c \rangle$ .

$u_{n-1}$	$u_{n-2}$	$\dots$	$u_2$	$u_1$	$u_0$
$v_{n-1}$	$v_{n-2}$		$v_2$	$v_1$	$v_0$
$w_{n-1}$	$w_{n-2}$		$w_2$	$w_1$	$w_0$
$c_{n-1}$	$c_{n-2}$	$c_{n-3}$	$\dots$	$c_1$	$c_0$
$0$	$s_{n-1}$	$s_{n-2}$		$s_2$	$s_1$
					$s_0$

Solved by juxtaposition of independent full adders (**not** in a chain!)

# Carry-save adder (also: 3:2 adder)

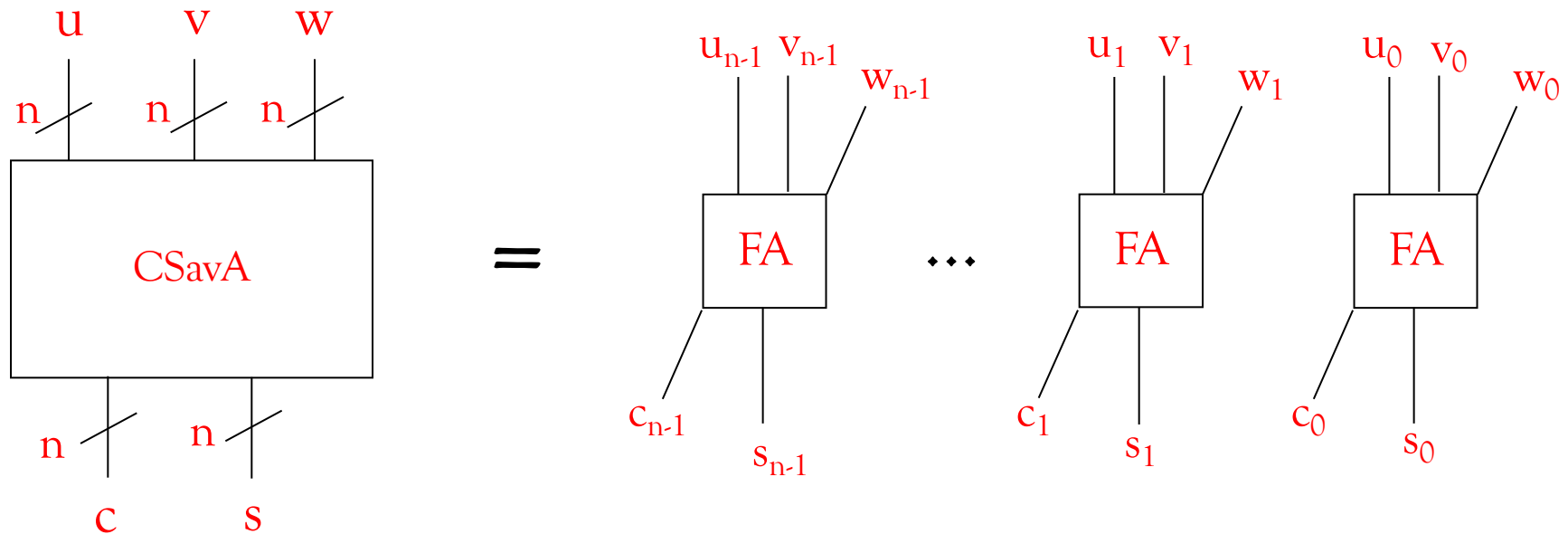


Cost:  $C(\text{CSavA}^n) = n \cdot C(\text{FA}) = 5 \cdot n$

Depth:  $\text{depth}(\text{CSavA}^n) = \text{depth}(\text{FA}) = 3$
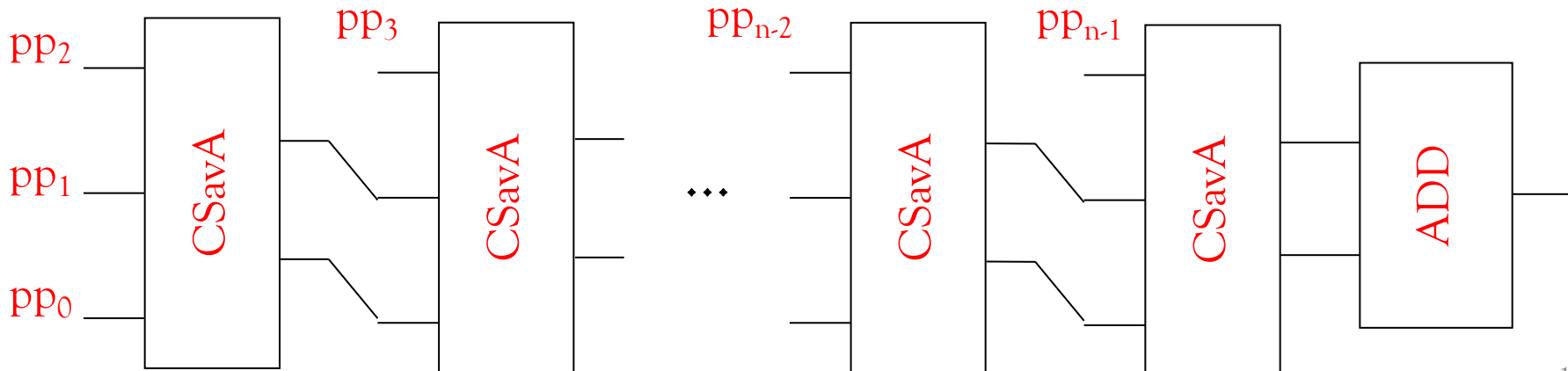
# 1. Serial solution

- Cascade connection of  $n-2$  CSavAs of length  $2n$ :
  - Combine  $n$  partial products into two  $2n$ -bit words
- Add the last two  $2n$ -bit words using a CLA
- Cost:  $O(n^2)$ , Depth:  $O(n)$






## 2. Tree-shaped solution


- Combine two carry-save adders to reduce **four  $2n$ -bit input words** into two output words: 4-to-2 reducer
- Balanced binary tree of **4-to-2 reducers** to summarize the  $n$  partial products using two  $2n$ -bit words
- Addition of the two final  $2n$ -bit words using a CLA

**Cost:**  $O(n^2)$

**Depth:**  $O(\log n)$

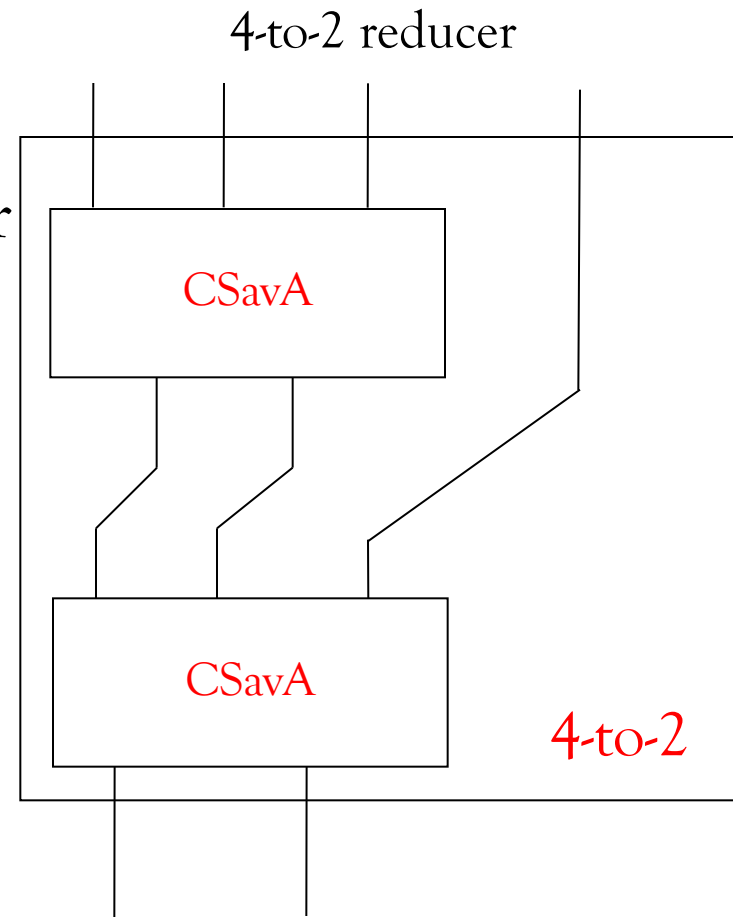
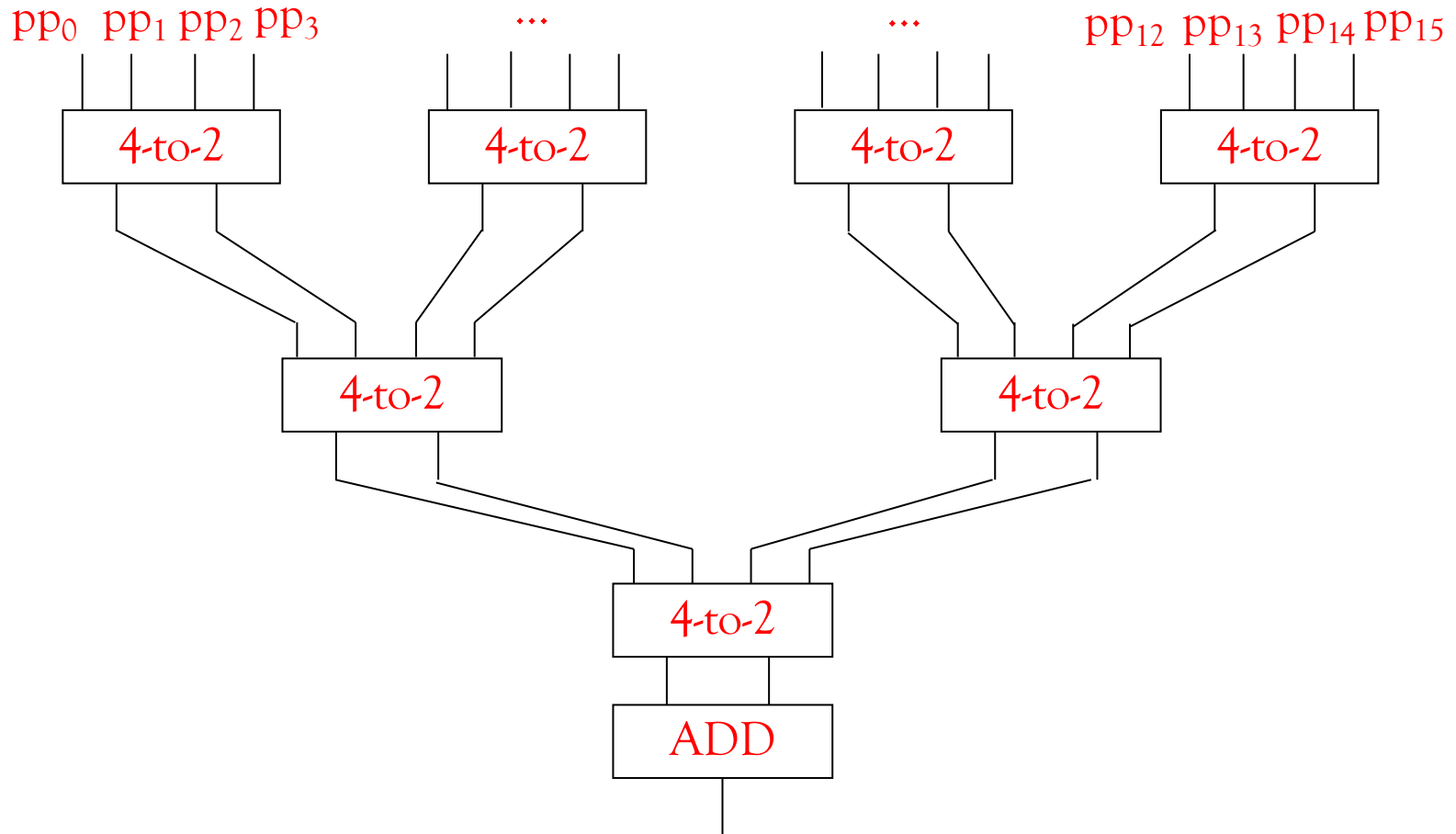
# Adder stage of the log-time multiplier for 16 bits




# Construction of an ALU

**ALU = arithmetic logic unit** for performing basic arithmetic and logic operations

Here:  $n$ -bit-ALU with:

- 2  $n$ -bit operands  $a$ ,  $b$ , carry-in  $c$
- $m$ -bit select input, which selects the function to execute
- $(n+1)$ -bit output

# Schematic of an n-bit ALU

 

# Example ALU specification

Here: 8 functions, i.e. 3-bit select input

Function number			ALU function
$s_2$	$s_1$	$s_0$	
0	0	0	$0 \dots 0$
0	0	1	$[b] - [a]$
0	1	0	$[a] - [b]$
0	1	1	$[a] + [b] + c$
1	0	0	$a \oplus b = (a_{n-1} \oplus b_{n-1}, \dots, a_0 \oplus b_0)$
1	0	1	$a \vee b = (a_{n-1} \vee b_{n-1}, \dots, a_0 \vee b_0)$
1	1	0	$a \wedge b = (a_{n-1} \wedge b_{n-1}, \dots, a_0 \wedge b_0)$
1	1	1	$1 \dots 1$

“Arithmetic”

“Logic”

# Possible implementations of an ALU

## 1. Possibility:

Implement  $f_0, \dots, f_{2^m-1}$  separately via circuits  $C_i$  for  $f_i$ ; then select correct output via generalized multiplexer


*(see upcoming figure)*

## 2. Possibility:


Shared circuit for similar functions

*(see upcoming figure)*

# 1. Possible implementation

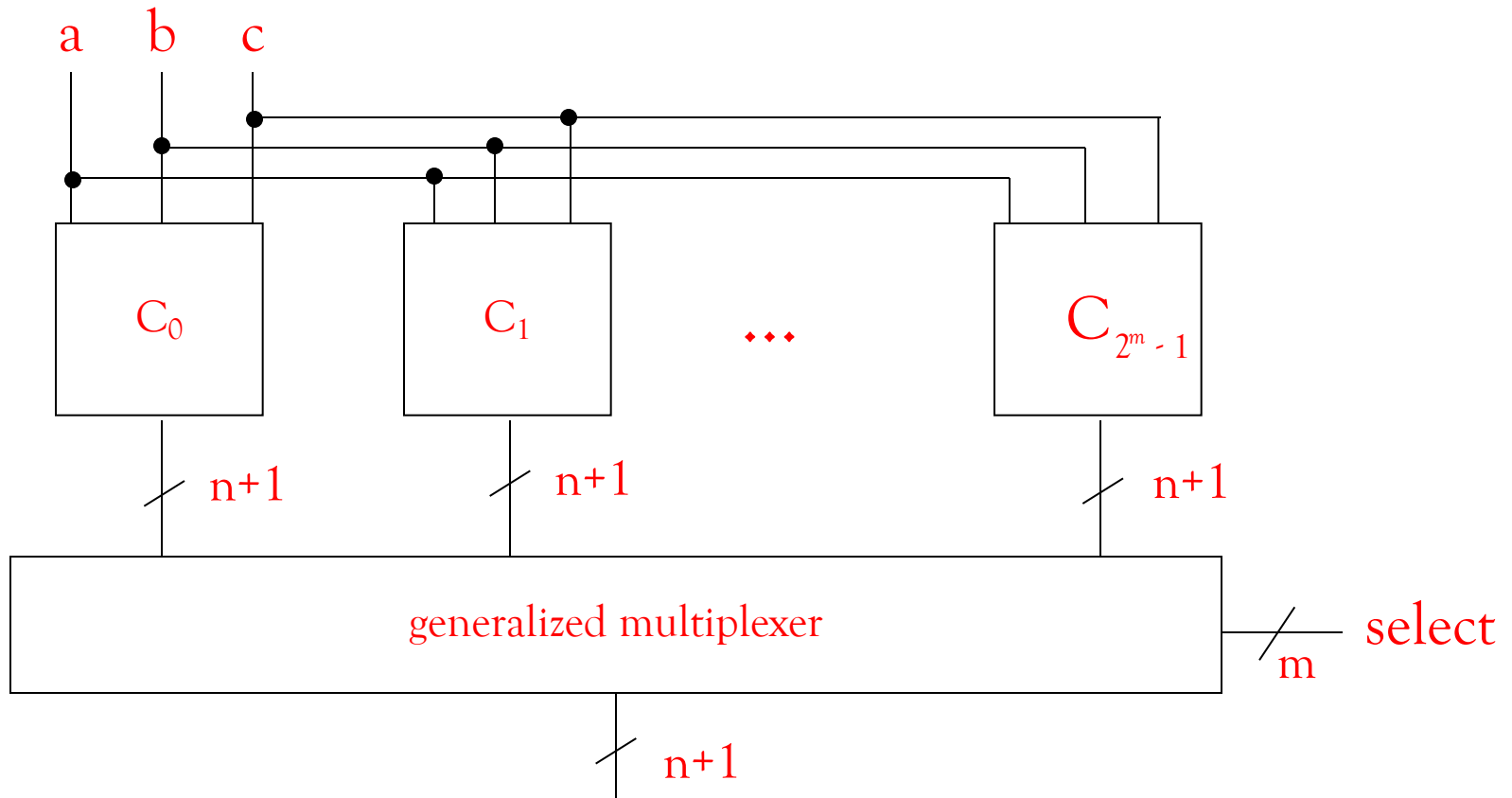

# 2. Possible implementation

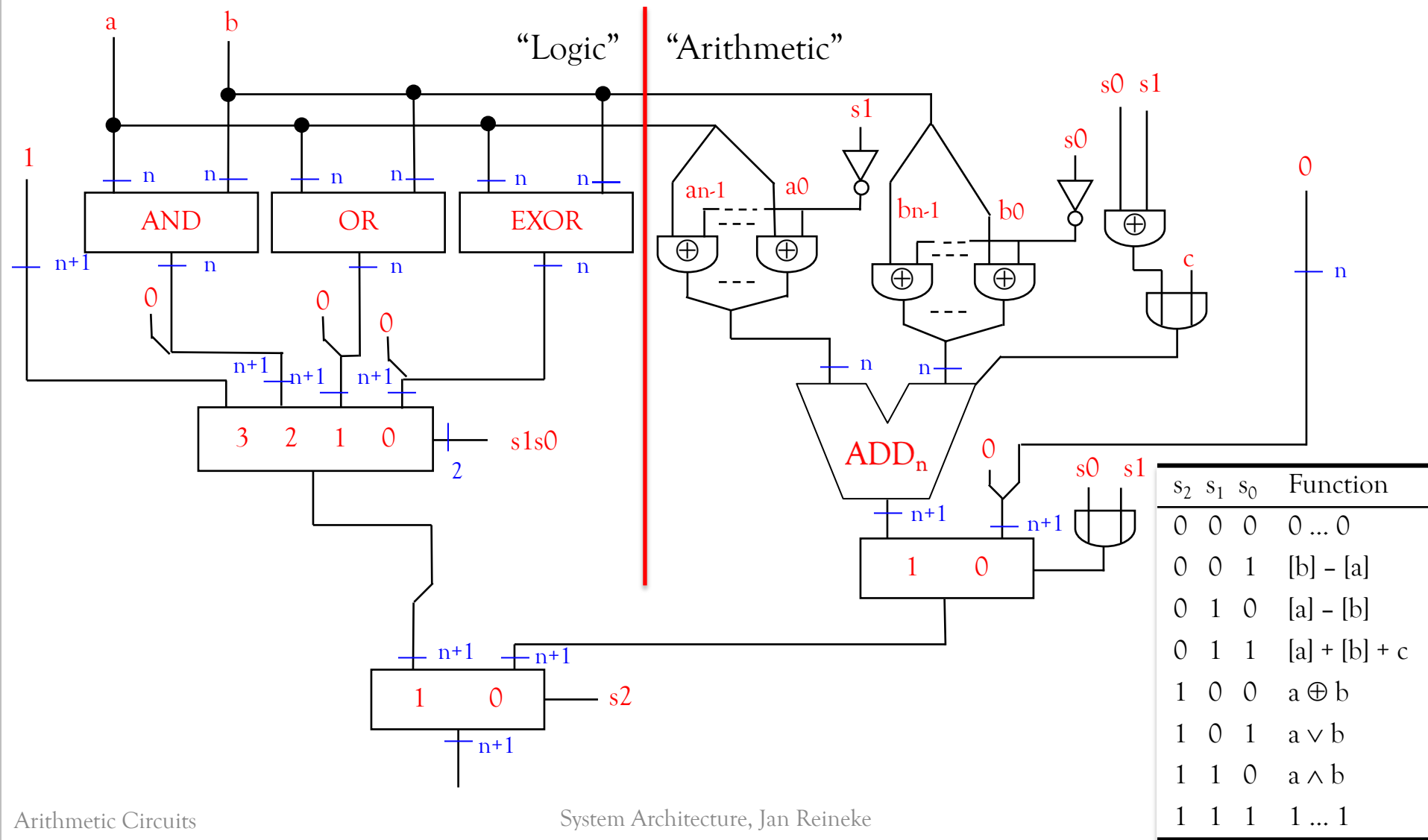



# Outlook:

## Datapath and instruction execution

