

# Hardware Description Languages: Verilog

Jan Reineke




UNIVERSITÄT  
DES  
SAARLANDES

## Step I: circuit design

- manual with paper and pencil
- at the level of individual transistors

# History: Hardware design in 1970

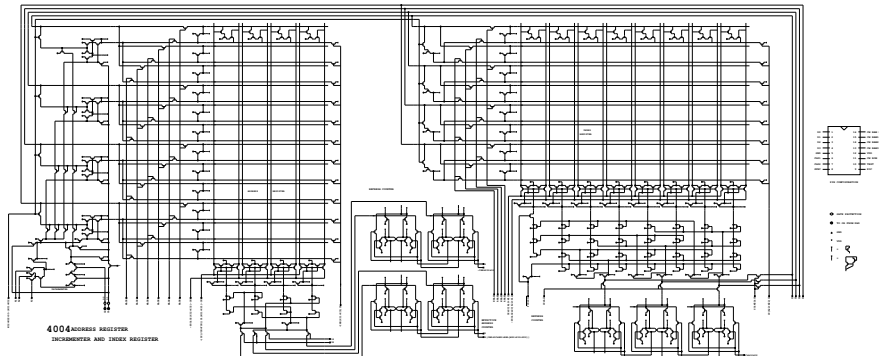*Example:* Intel 4004, 2.300 transistors, 108KHz, 10 $\mu$ m (excerpt)  
first mass-produced single-chip microprocessor!



<http://www.4004.com/assets/redrawn-4004-schematics-2006-11-12.pdf>  
Re-drawn schematics based on Revision G of the original Intel 4004 schematics by Intel Corporation (August 6, 1976). Schematic capture and design verification by Fred Huettig, Brian Silverman and Barry Silverman (February 2, 2006).

## Step I: circuit design

- manual with paper and pencil
- at the level of individual transistors

## Step II: Fabrication of photomasks for lithographic process

- manual labor
- error prone

## History: Hardware design in 1970



Photo courtesy of the Intel Corporation, as published on  
<http://www.computerhistory.org/revolution/digital-logic/12/287/1614>

## Hardware description languages

- Abstract from transistors
- Simulation
- Hardware synthesis
  - using computer-aided design (CAD) programs
    - ▶ Field Programmable Gate Array (FPGA)
    - ▶ Application-Specific Integrated Circuit (ASIC)

## Hardware description languages

- Abstract from transistors
- Simulation
- Hardware synthesis
  - using computer-aided design (CAD) programs
    - ▶ Field Programmable Gate Array (FPGA)
    - ▶ Application-Specific Integrated Circuit (ASIC)

In this course, we use . . .

**Verilog**, originally developed by Gateway Design Automation in 1984

Other languages: VHDL, SystemVerilog, Chisel

# Previous concepts in the course



# Previous concepts in the course

Boolean functions  $\mathbb{B}^n \rightarrow \mathbb{B}^m$

Boolean expressions  $a \wedge b$

Combinatorial circuits

Boolean functions  $\mathbb{B}^n \rightarrow \mathbb{B}^m$

Boolean expressions  $a \wedge b$

Combinatorial circuits

Moore/Mealy automata


Memory elements (Flip-Flops, SRAM, ...)

Sequential circuits

- 1 Introduction
- 2 Verilog for Hardware Synthesis
  - Combinatorial circuits
  - Sequential circuits
- 3 Simulation
  - Test benches
- 4 *Optional*: FPGA and Synthesis

# Modules

## Encapsulation of circuits

 

```

module name(
    input a,
    input [1:0] b,
    input c,
    output y
);

// functionality

endmodule
  
```

# Assignments and Bitwise operators

- Assignment of signals via `assign` and `=`
- Bitwise operators correspond to gates  
And `&`, Or `|`, Negation `~`, Xor `^`

*Example:* Half adder

# Assignments and Bitwise operators

- Assignment of signals via `assign` and `=`
- Bitwise operators correspond to gates  
And `&`, Or `|`, Negation `~`, Xor `^`

*Example:* Half adder

```
module halfadder(  
    input a,  
    input b,  
    output s,  
    output c  
);
```

```
endmodule
```

# Assignments and Bitwise operators

- Assignment of signals via `assign` and `=`
- Bitwise operators correspond to gates  
And `&`, Or `|`, Negation `~`, Xor `^`

*Example:* Half adder

```
module halfadder(  
    input a,  
    input b,  
    output s,  
    output c  
);  
    assign s = a ^ b;  
    assign c = a & b;  
endmodule
```

- General form  $N'Bw$ 
  - ▶  $N$  number of bits
  - ▶  $B$  basis of the numeral system
  - ▶  $w$  sequence of numerals (digits)



- General form  $N'Bw$ 
  - ▶  $N$  number of bits (*independently* (!) of the employed numeral system)
  - ▶  $B$  basis of the numeral system
  - ▶  $w$  sequence of numerals (digits)

- General form  $N' Bw$ 
  - ▶  $N$  number of bits (*independently* (!) of the employed numeral system)
  - ▶  $B$  basis of the numeral system
  - ▶  $w$  sequence of numerals (digits)
  
- Examples:
  - ▶ binary numbers 4' b1011
  - ▶ long binary numbers 8' b1010\_0011
  - ▶ *without* number of bits ' b101
  - ▶ decimal 4' d5
  - ▶ hexadecimal 8' ha3
  - ▶ signed decimal number -3' sd5 (s for “signed”)

- General form  $N' Bw$ 
  - ▶  $N$  number of bits (*independently* (!) of the employed numeral system)
  - ▶  $B$  basis of the numeral system
  - ▶  $w$  sequence of numerals (digits)
  
- Examples:
  - ▶ binary numbers 4' b1011
  - ▶ long binary numbers 8' b1010\_0011
  - ▶ *without* number of bits ' b101
  - ▶ decimal 4' d5
  - ▶ hexadecimal 8' ha3
  - ▶ signed decimal number -3' sd5 (s for “signed”)
  
- Don't-care values 3' b1xx (e.g. irrelevant signals in the MIPS decoder)
  - ▶ Simulation: simplifies debugging
  - ▶ Synthesis: more flexibility

# Comparison and selection operators

- bit-by-bit (in)equality `==`, `!=`
- unsigned comparison of values `<`, `<=`, ...
- ternary operator `a ? b : c`

*Example:* 4-bit multiplexer

# Comparison and selection operators

- bit-by-bit (in)equality `==`, `!=`
- unsigned comparison of values `<`, `<=`, ...
- ternary operator `a ? b : c`

*Example:* 4-bit multiplexer

```
module multiplexer(  
    input s,  
    input [3:0] x0,  
    input [3:0] x1,  
    output [3:0] y  
);  
  
endmodule
```

# Comparison and selection operators

- bit-by-bit (in)equality `==`, `!=`
- unsigned comparison of values `<`, `<=`, ...
- ternary operator `a ? b : c`

*Example:* 4-bit multiplexer


```
module multiplexer(  
    input s,  
    input [3:0] x0,  
    input [3:0] x1,  
    output [3:0] y  
);  
    assign y = (s == 1'b0) ? x0 : x1;  
endmodule
```

## Instantiating modules

```
modulename instancename (  
    .param1name (arg1name) ,  
    .param2name (arg2name) ,  
    ...  
);
```

Temporary signals via `wire`

# Example: Full adder

 




# Example: Full adder

```

module fulladder(
  input a0,
  input b0,
  input c,
  output s0,
  output s1
);

```

 

```

endmodule

```

# Example: Full adder

```


module fulladder(
  input a0,
  input b0,
  input c,
  output s0,
  output s1
);
  wire ha0c, ha0s, ha1c;

```

```

endmodule

```

 


# Example: Full adder

```


module fulladder(
  input a0,
  input b0,
  input c,
  output s0,
  output s1
);
  wire ha0c, ha0s, ha1c;
  halfadder ha0(.a(a0), .b(b0), .c(ha0c), .s(ha0s));

  endmodule
  
```

 

 
## Example: Full adder

```
module fulladder(  
    input a0,  
    input b0,  
    input c,  
    output s0,  
    output s1  
);  
    wire ha0c, ha0s, ha1c;  
    halfadder ha0(.a(a0), .b(b0), .c(ha0c), .s(ha0s));  
    halfadder ha1(.a(ha0s), .b(c), .c(ha1c), .s(s0));  
endmodule
```



## Example: Full adder

```
module fulladder(  
    input a0,  
    input b0,  
    input c,  
    output s0,  
    output s1  
);  
    wire ha0c, ha0s, ha1c;  
    halfadder ha0(.a(a0), .b(b0), .c(ha0c), .s(ha0s));  
    halfadder ha1(.a(ha0s), .b(c), .c(ha1c), .s(s0));  
    assign s1 = ha0c | ha1c;  
endmodule
```

 

- Part-selects of `a[7:0]`

`a[2]` or `a[1:0]` or `a[3 +: 4]` (= `a[6:3]`)

- Part-selects of  $a[7:0]$   
 $a[2]$  or  $a[1:0]$  or  $a[3 +: 4]$  ( $= a[6:3]$ )
- If e.g.  $a[7:0] = 10011011$   
Then  $a[2] = 0$ ,  $a[1:0] = 11$ , and  $a[6:3] = 0011$ .

- Shift operation, logical (fills with zero)  $\ll$ ,  $\gg$   
E.g.  $1010 \gg 1 = 0101$



- Shift operation, logical (fills with zero)  $\ll$ ,  $\gg$   
E.g.  $1010 \gg 1 = 0101$
- Shift operation, arithmetic (keep sign)  $\lll$ ,  $\ggg$   
E.g.  $1010 \ggg 1 = 1101$

- Shift operation, logical (fills with zero)  $\ll$ ,  $\gg$   
E.g.  $1010 \gg 1 = 0101$
- Shift operation, arithmetic (keep sign)  $\lll$ ,  $\ggg$   
E.g.  $1010 \ggg 1 = 1101$
- In practice,  $\lll$  and  $\ll$  behave the same.

- Reduction  $\&a$  of  $a[7:0]$   
is equivalent to  $a[7] \& a[6] \& \dots \& a[0]$

- Reduction `&a` of `a[7:0]`  
is equivalent to `a[7] & a[6] & ... & a[0]`
- arithmetic operators (unsigned) `+`, `*`, `...`

- Reduction  $\&a$  of  $a[7:0]$   
is equivalent to  $a[7] \& a[6] \& \dots \& a[0]$
- arithmetic operators (unsigned)  $+$ ,  $*$ ,  $\dots$
- Concatenation of  $a$  and  $b$  into  $c[1:0]$   
`assign c[1:0] = {a, b};`

- Reduction &a of  $a[7:0]$   
is equivalent to  $a[7] \& a[6] \& \dots \& a[0]$
- arithmetic operators (unsigned)  $+$ ,  $*$ ,  $\dots$
- Concatenation of  $a$  and  $b$  into  $c[1:0]$   
`assign c[1:0] = {a, b};`
- Duplication of bits  $c[31:0] = \{16\{2'b10\}\}$   
 $= c[31:0] = 10$

## 1 Introduction

## 2 Verilog for Hardware Synthesis

- Combinatorial circuits
- Sequential circuits

## 3 Simulation

- Test benches

## 4 *Optional:* FPGA and Synthesis

Two types of memories:

- level-triggered latches
- edge-triggered flip-flops



Two types of memories:

- level-triggered latches
- edge-triggered flip-flops

Both types of memory are *in principle* supported by Verilog, but not by all synthesis tools

⇒ We are only using edge-triggered flip-flops

- Declaration of variable that can be used as a 1-bit memory:


```
reg q;
```

- `always` block for assignment of `reg` variables.  
Execution depends on variables in *sensitivity list*.

```
always @(sensitivity list)
begin
    ...
end
```

- Edge detection `posedge a` and `negedge a`
- (Non-blocking) assignment `<=`
- Common structuring elements within an `always` block: `if`, `case`

 
## Example 1: D-Flip-Flop with enable input



```
module dffe(  
    input clk,  
    input din,  
    input enable,  
    output out  
);
```

```
endmodule
```
 
# Example 1: D-Flip-Flop with enable input



```

module dffe(
    input clk,
    input din,
    input enable,
    output out
);
    reg q;


```

```

endmodule

```
 
## Example 1: D-Flip-Flop with enable input




```

module dffe(
    input clk,
    input din,
    input enable,
    output out
);
    reg q;
    always @(posedge clk)
    begin

        end

    endmodule
  
```
 
## Example 1: D-Flip-Flop with enable input




```

module dfpe(
    input clk,
    input din,
    input enable,
    output out
);
    reg q;
    always @(posedge clk)
    begin
        if (enable)
            q <= din;
    end

endmodule

```
 
## Example 1: D-Flip-Flop with enable input



```

module dfpe(
    input clk,
    input din,
    input enable,
    output out
);
    reg q;
    always @(posedge clk)
    begin
        if (enable)
            q <= din;
    end
    assign out = q;
endmodule
  
```

## Example II: Cyclic 4-bit counter

```
module counter (  
    input clock,  
    input reset,  
    output [3:0] count  
);  
    reg [3:0] q;  
    always @(posedge clock)  
    begin  
        if (reset)  
            q <= 4'b0;  
        else  
            q <= q + 1'b1;  
        end  
    assign count = q;  
endmodule
```



## Example II: Cyclic $n$ -bit counter

```
module counter #(parameter N = 4) (  
    input clock,  
    input reset,  
    output [N-1:0] count  
);  
    reg [N-1:0] q;  
    always @(posedge clock)  
    begin  
        if (reset)  
            q <= 'b0;  
        else  
            q <= q + 1'b1;  
        end  
        assign count = q;  
    endmodule
```

# Outlook: always for combinatorial circuits

```
wire x, y;  
assign x = a ? b : c;  
assign y = a ? b : d ? c : e;
```

```
wire x, y;  
assign x = a ? b : c;  
assign y = a ? b : d ? c : e;
```

```
reg x, y;  
always @*  
begin  
    if (a) begin  
        x = b;  
        y = b;  
    end else begin  
        x = c;  
        if (d)  
            y = c;  
        else  
            y = e;  
    end  
end
```

⇒ reg and always can also be used for combinatorial circuits

# Blocking and non-blocking assignments

## Blocking assignment

```
reg x, y;  
always @(posedge clk)  
begin  
    x = y;  
    y = x;  
end
```

Assignments are blocking,  
i.e., they are executed **sequentially**  
⇒  $x$  and  $y$  are equal

## Non-blocking assignment

```
reg x, y;  
always @(posedge clk)  
begin  
    x <= y;  
    y <= x;  
end
```

Assignments are non-blocking, i.e.,  
are conceptually executed in parallel  
⇒  $x$  and  $y$  are exchanged

- 1 For memory elements use always `@(pos/negedge clk)`,  
non-blocking assignments `<=` and `reg`
- 2 For simple combinatorial circuits `assign`,  
blocking assignments `=` and `wire`
- 3 For complex combinatorial circuits always `@*`,  
blocking assignments `=` and `reg`
- 4 Never assign a signal multiple times (`wire` or `reg`),  
i.e., no two *active* assignments at the same time

- 1 For memory elements use always `@(pos/negedge clk)`,  
non-blocking assignments `<=` and `reg`
- 2 For simple combinatorial circuits `assign`,  
blocking assignments `=` and `wire`
- 3 For complex combinatorial circuits always `@*`,  
blocking assignments `=` and `reg`
- 4 Never assign a signal multiple times (`wire` or `reg`),  
i.e., no two *active* assignments at the same time

Follow these rules

⇒ Otherwise: *strange* often, subtle errors

## 1 Introduction

## 2 Verilog for Hardware Synthesis

- Combinatorial circuits
- Sequential circuits

## 3 Simulation

- Test benches

## 4 *Optional:* FPGA and Synthesis

A **test bench** is a Verilog module that

- 1 instantiates a module-under-test  $M$ ,
- 2 generates input stimuli for  $M$ , and
- 3 *optionally* tests the correctness of the outputs of  $M$  automatically.



Use of *delays*:

```
statement 1; #5; statement 2; delays the sequential execution
```

Use of *delays*:

statement 1; #5; statement 2; **delays the sequential execution**

- Once

```
initial
begin
  reset <= 1;
  #22;
  reset <= 0;
end
```

## Use of *delays*:

statement 1; #5; statement 2; **delays the sequential execution**

### ■ Once

```
initial
begin
  reset <= 1;
  #22;
  reset <= 0;
end
```

### ■ Periodically

```
always
begin
  clk <= 1; #5; clk <= 0; #5;
end
```

## Use of *delays*:

statement 1; #5; statement 2; **delays the sequential execution**

### ■ Once

```
initial
begin
  reset <= 1;
  #22;
  reset <= 0;
end
```

### ■ Multiple times with repeat (x)

### ■ Periodically

```
always
begin
  clk <= 1; #5; clk <= 0; #5;
end
```

Additional functions to control the simulation, **non-synthesizable**, thus mainly used in test benches

- `$display` output similar to `printf` in C
- `$finish` stops the simulation
- `$readmemb/$readmemh` initializes memory elements
- `$dumpfile/$dumpvars` outputs variables as waveforms

**Icarus**: open-source simulator for Verilog

<http://iverilog.icarus.com/>

**GTKWave**: open-source visualization and analysis tool for waveforms

<http://gtkwave.sourceforge.net/>

**Icarus**: open-source simulator for Verilog

<http://iverilog.icarus.com/>

**GTKWave**: open-source visualization and analysis tool for waveforms

<http://gtkwave.sourceforge.net/>

# Demo

## 1 Introduction

## 2 Verilog for Hardware Synthesis

- Combinatorial circuits
- Sequential circuits


## 3 Simulation

- Test benches

## 4 *Optional:* FPGA and Synthesis




## ■ Look-up table (4LUT)

 


Can be used to implement an arbitrary Boolean function from  $\mathbb{B}^4 \rightarrow \mathbb{B}$ .

## ■ Register

 

 
# Structure of a Field Programmable Gate Array<sup>1</sup>




*In addition:* Dedicated components:

Memory blocks (8192 Bits), multipliers (9 Bits), etc.
 
<sup>1</sup>[http://commons.wikimedia.org/wiki/File:Fpga\\_structure.svg](http://commons.wikimedia.org/wiki/File:Fpga_structure.svg)



 

- 1 Analysis and elaboration
  - ▶ Syntax and semantics
  - ▶ Find dedicated components
- 2 Synthesis
  - ▶ Translation into logical blocks
- 3 Fitter
  - ▶ Place-and-Route
- 4 Assembler
- 5 Timing analysis
  - ▶ Computation of critical paths and maximal frequency

## Example: Pong



[https://commons.wikimedia.org/wiki/File:APF\\_TV\\_Fun\\_\(with\\_paddle\\_model\).jpg](https://commons.wikimedia.org/wiki/File:APF_TV_Fun_(with_paddle_model).jpg)

Original from: <http://www.flickr.com/photos/adampsyche/3085132136/>

# Brainstorming: Pong game logic

State?

Behavior?

State?

- Position of left paddle
- Position of right paddle
- Position/speed of ball

Behavior?



## State?

- Position of left paddle
- Position of right paddle
- Position/speed of ball

## Behavior?

- Collision paddles
- Collision borders

# Brainstorming: Pong game logic

## State?

- Position of left paddle
- Position of right paddle
- Position/speed of ball

## Behavior?

- Collision paddles
- Collision borders

## Verilog implementation:

<https://github.com/tdudziak/fpga-pong>

- Retro games <http://bit.ly/1r9EMks>
- Signal processing
- Hardware Prototyping
- Encryption of network traffic <http://bit.ly/WkzpcE>
- Parallel algorithms <http://bit.ly/ZYOTJG>,  
DES attack (2003) <http://bit.ly/11ZKxze>
- Earlier: Bitcoin mining (now: ASICs)