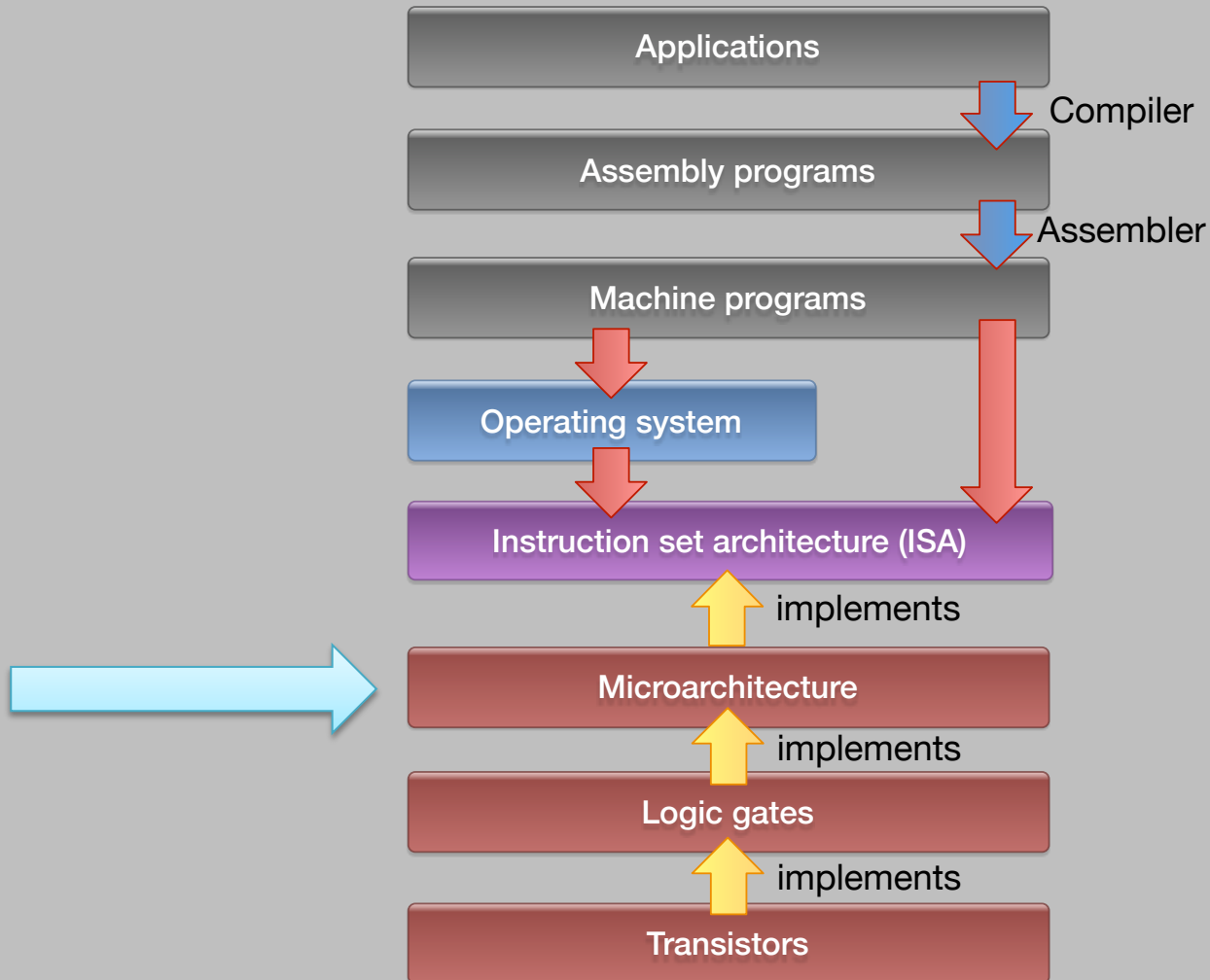


# Microarchitecture at the Example of MIPS

Becker/Molitor, Chapter 10 treats a similar but not identical system.  
We follow the American book "Digital design and computer architecture"  
by Harris and Harris, 2013.  
Here, Chapters 6 and 7 are particularly relevant.

Jan Reineke  
Universität des Saarlandes

# Abstraction layers in computer systems



# Overview: Architecture vs Microarchitecture


## Microarchitecture

= concrete implementation of an instruction set in hardware

= „How“ a computer works

*For example:* Intel Skylake, AMD Zen 3 (both x86), Apple M1 (ARM)

# High-level Structure

 

## Datapath:


- Processing and transport of instructions and data
- Must support all operations and data transports
- Many options of differing complexity and speed are possible

## Control:

- Processing and transport of control signals
- Many options:
  - Purely combinatorial control (here)
  - State-based control (e.g. with Pipelining, more about this later)
  - Microprogrammed (in current Intel and AMD processors)
 
# Instruction encoding

- **Instruction encoding** refers to the encoding of instructions in machine words.
- MIPS uses a fixed-length 32-bit encoding of all instructions (this is unlike, e.g. x86)
- We distinguish three types I, J and R:



# Instruction encoding

Abbreviation	Meaning
I	immediate
J	jump
R	register
op	6-bit encoding of the operation
rs	5-bit encoding of a source register
rt	5-bit encoding of a source or target register
immediate	16-bit immediate value
target	26-bit jump target
rd	5-bit encoding of the target register
shamt	5-bit encoding of “shift amount”
funct	6-bit encoding of the function

# The MIPS subset

- R-type instructions:

```

add          add rd, rs, rt
subtract     sub rd, rs, rt
AND          and rd, rs, rt
OR           or rd, rs, rt
set less than  slt rd, rs, rt
  
```

op code				Function	
000000	rs	rt	rd	00000	100000
000000	rs	rt	rd	00000	100010
000000	rs	rt	rd	00000	100100
000000	rs	rt	rd	00000	100101
000000	rs	rt	rd	00000	101010

- Memory instructions:

```

load word    lw rt, imm(rs)
store word   sw rt, imm(rs)
  
```

100011	rs	rt	imm
101011	rs	rt	imm

- Jump and branch instructions:

```

branch on equal  beq rs, rt, imm
jump             j target
  
```


000100	rs	rt	imm
000010	target		

# Petri nets

We are describing the refinement of the instructions via **Petri nets**.  
Petri nets are a standard notation to represent parallel and distributed processes.
 
## Static representation:

- Petri nets consist of **places** and **transitions**, which are connected via edges.
- Transitions can be associated with **conditions** and **operations**.
- A Petri net graph must be bipartite, i.e., no two places may be directly connected. The same holds for transitions.






# Petri nets

## Dynamic representation:

- Places are associated with **tokens**.
- **Tokens** are “transported” across transitions according to the following rules:
  - A transition is “**enabled**” if
    - (a) the condition associated with the transition is satisfied, and
    - (b) every input place of the transition contains at least one token.
  - An enabled transition may “**fire**”.  
Then, one token is removed from each input place,  
and one token is added to each output place.  
And the operation associated with the transition is executed.


# Petri nets: Example

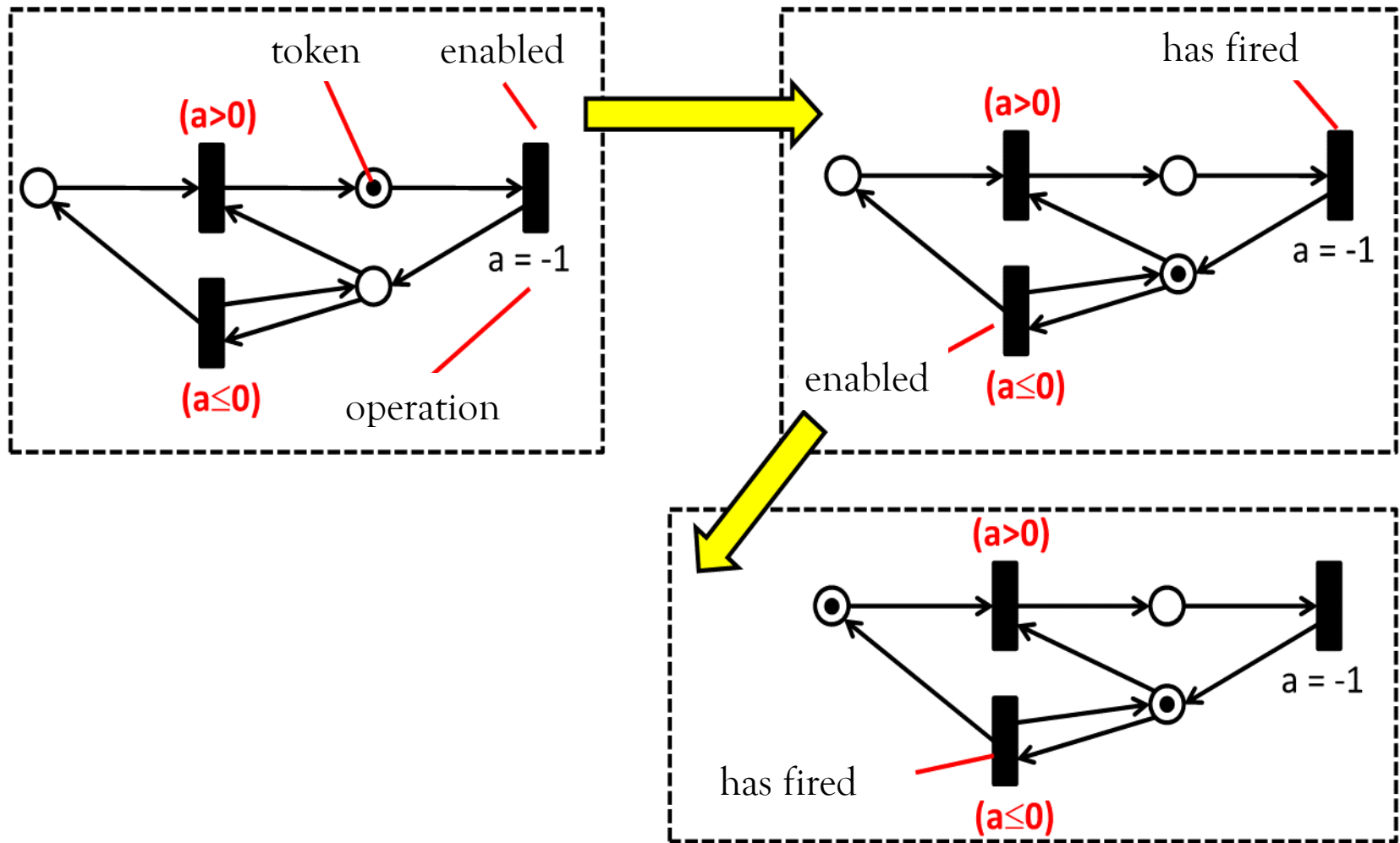

# Modeling the MIPS instructions

- **Temporary variables** to store 32-bit data and instructions:  
A, B, ALUOut, Target,  
PC (program counter), NPC (next program counter), IR (instruction)
- **Internal registers** of the processor:  $\text{Reg}[i], 0 \leq i < 32$
- **Memory** at the address  $i$ :  $\text{Mem}[i]$
- **Shifting** a word by 2 bit to the left:  
 $'01110' \ll 2 = '0111000'$
- **Concatenation** of bits:  $'001' \llcorner \lrcorner '110' = '001110'$
- **Extension** of a halfword into a word with/without sign extension:  
 $\text{SignExt}(), \text{ZeroExt}()$
- **Arithmetic operation** where  $\text{op}$  is from  $\{\text{'add'}, \text{'subtract'}, \text{'AND'}, \text{'OR'}, \text{'setOnLessThan'}\}$ :  $\text{ALU}(a, b, \text{op})$

# Example: R-type instructions

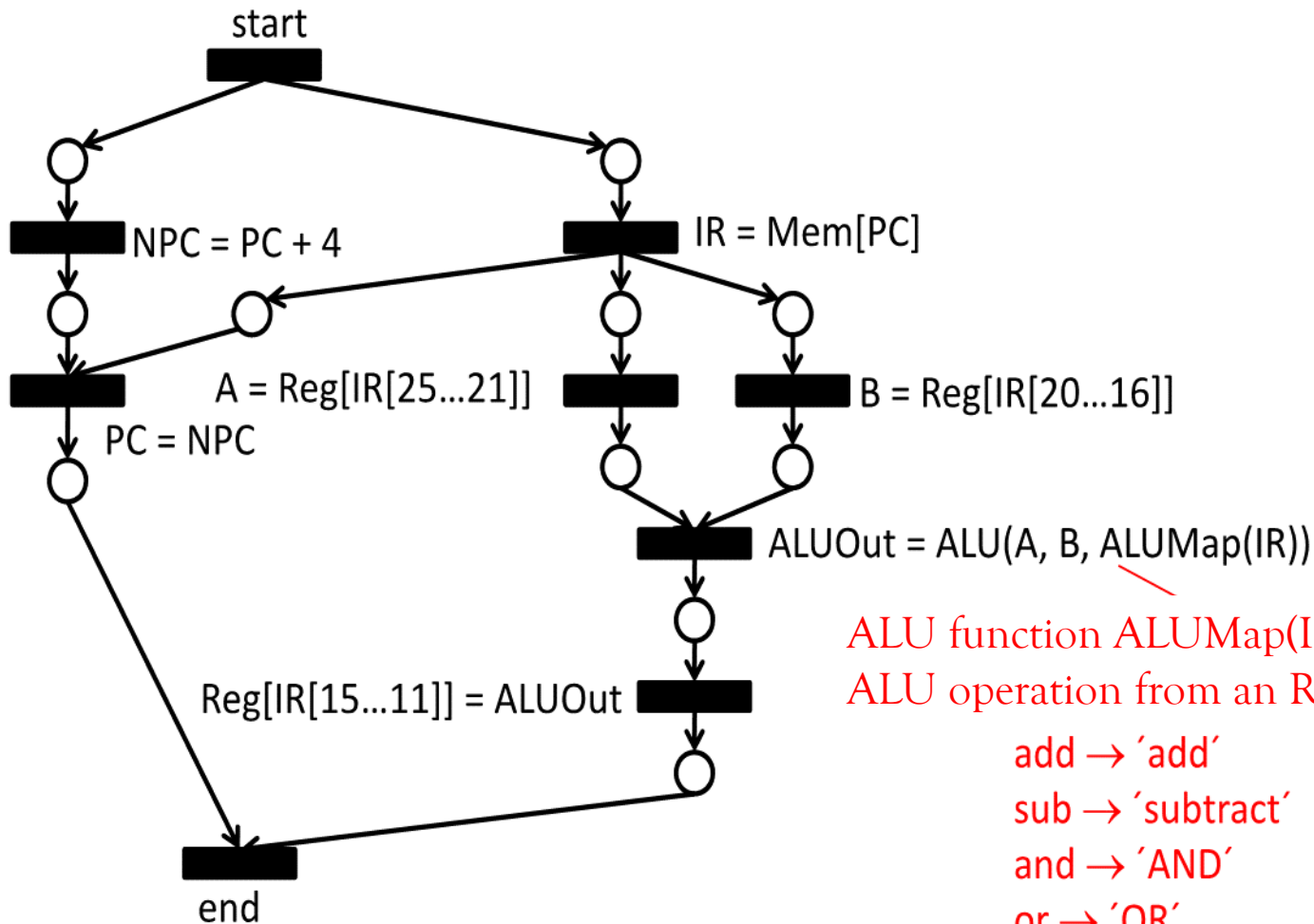

ALU function  $ALUMap(IR)$  determines the ALU operation from an R-type instruction:

add  $\rightarrow$  'add'


sub  $\rightarrow$  'subtract'

and  $\rightarrow$  'AND'


or  $\rightarrow$  'OR'

slt  $\rightarrow$  'setOnLessThan'


# Example: beq instruction

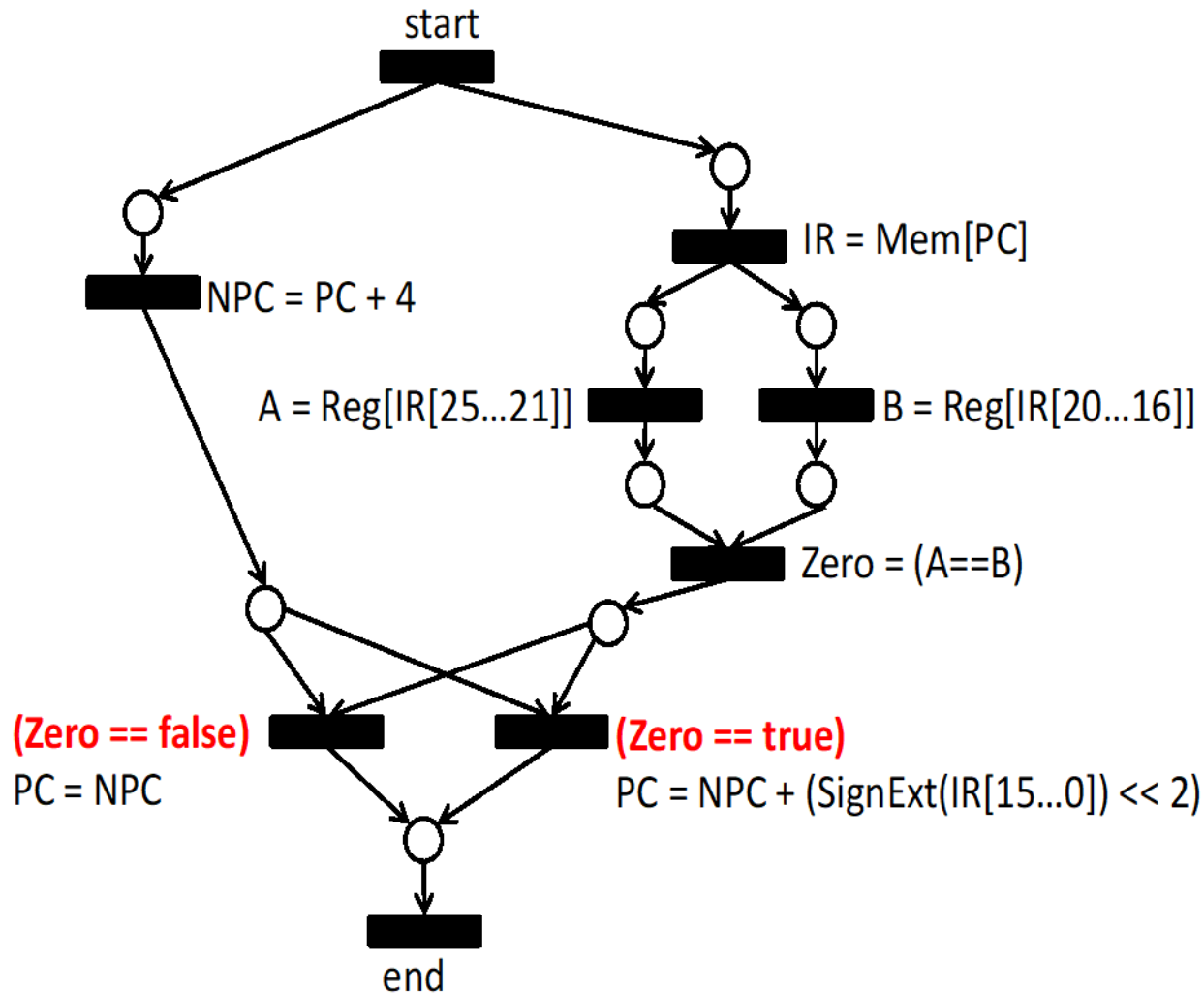


# Example: j instruction

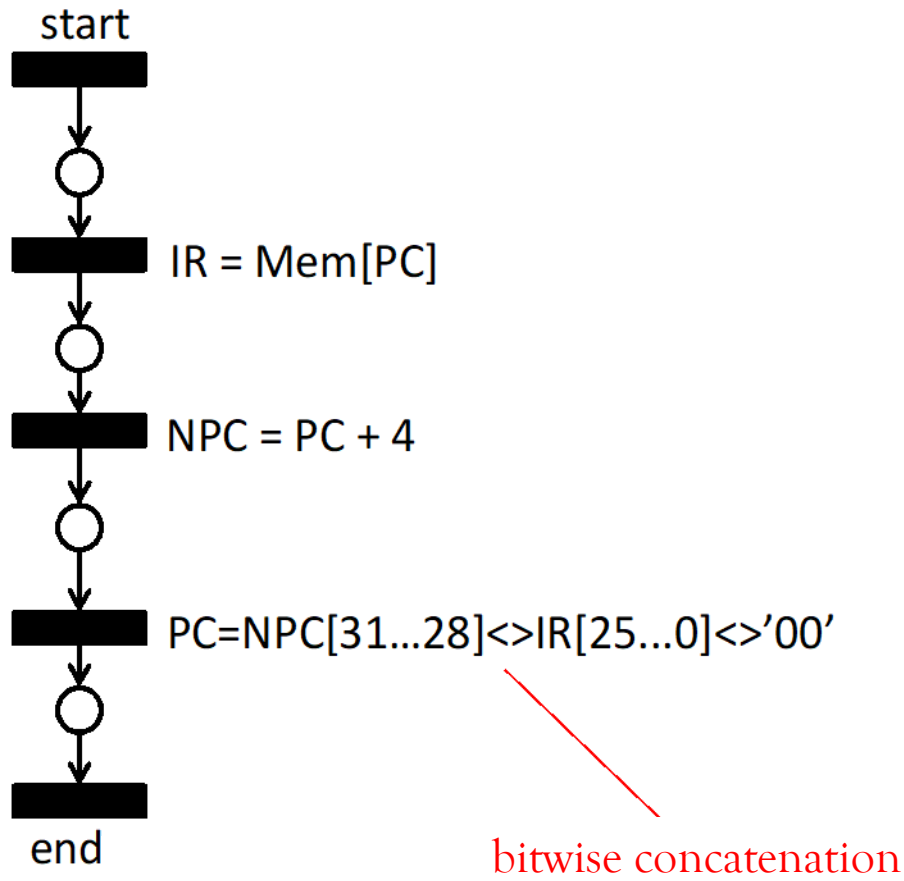

# Example: lw instruction

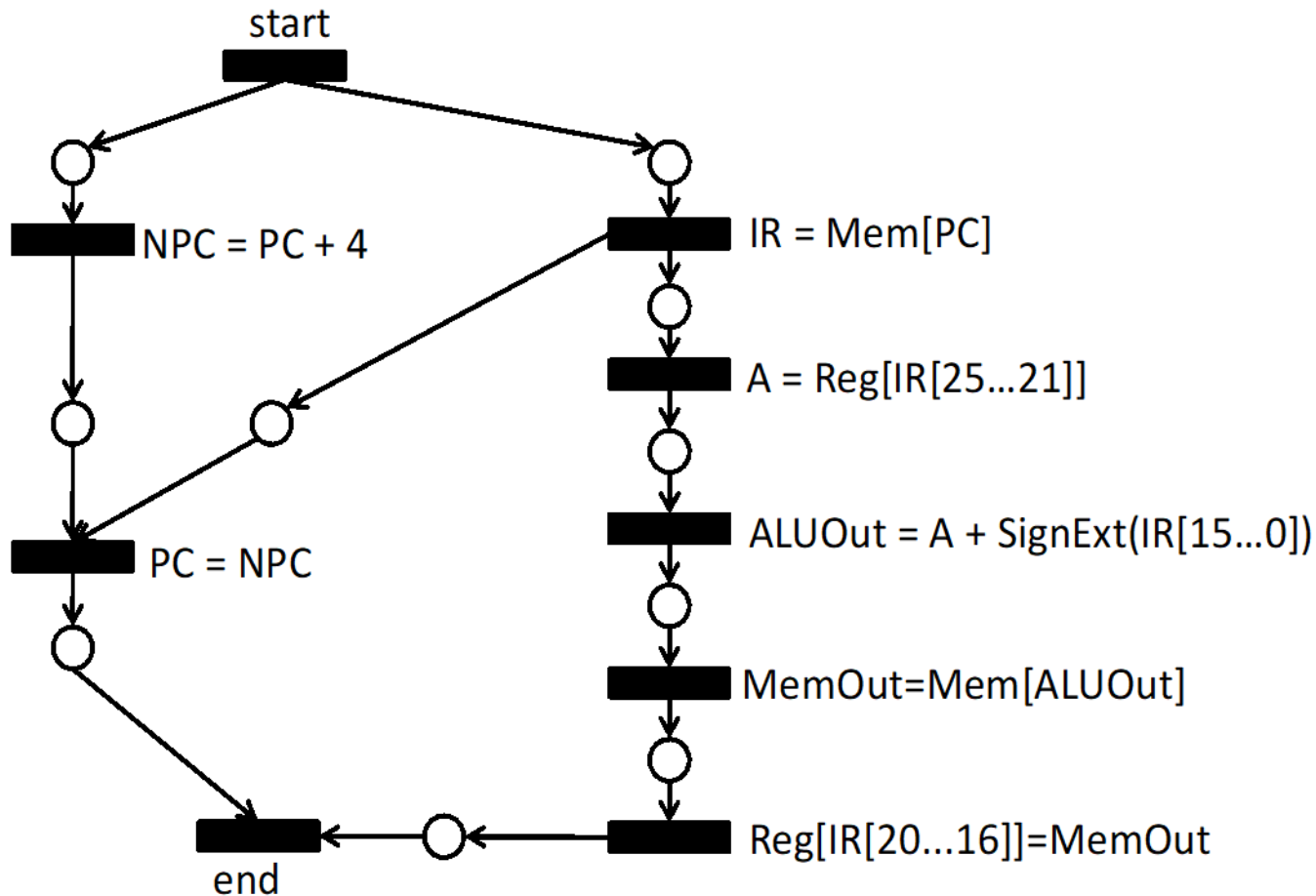

# Example: sw instruction

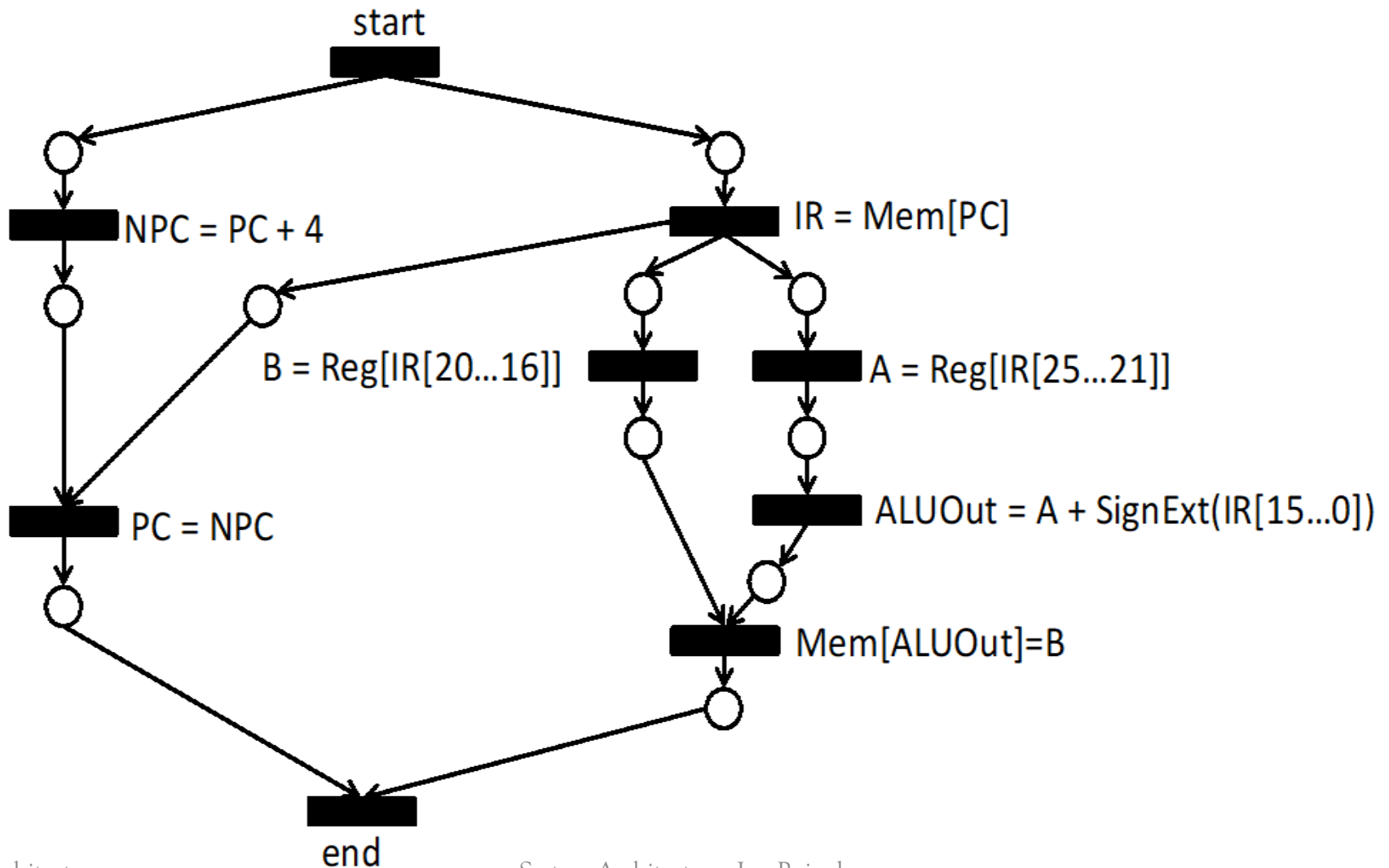




# Modeling the MIPS subset


## Unified Petri net:

- Merging the Petri nets of all instructions
- Definition of an additional temporary variable 'Target'.
- Connecting 'start' and 'end' for cyclic operation
- $Op[IR]$  from  $\{ 'R', 'lw', 'sw', 'beq', 'j' \}$  defines the type of instruction and is determined from  $IR[31..26]$ .
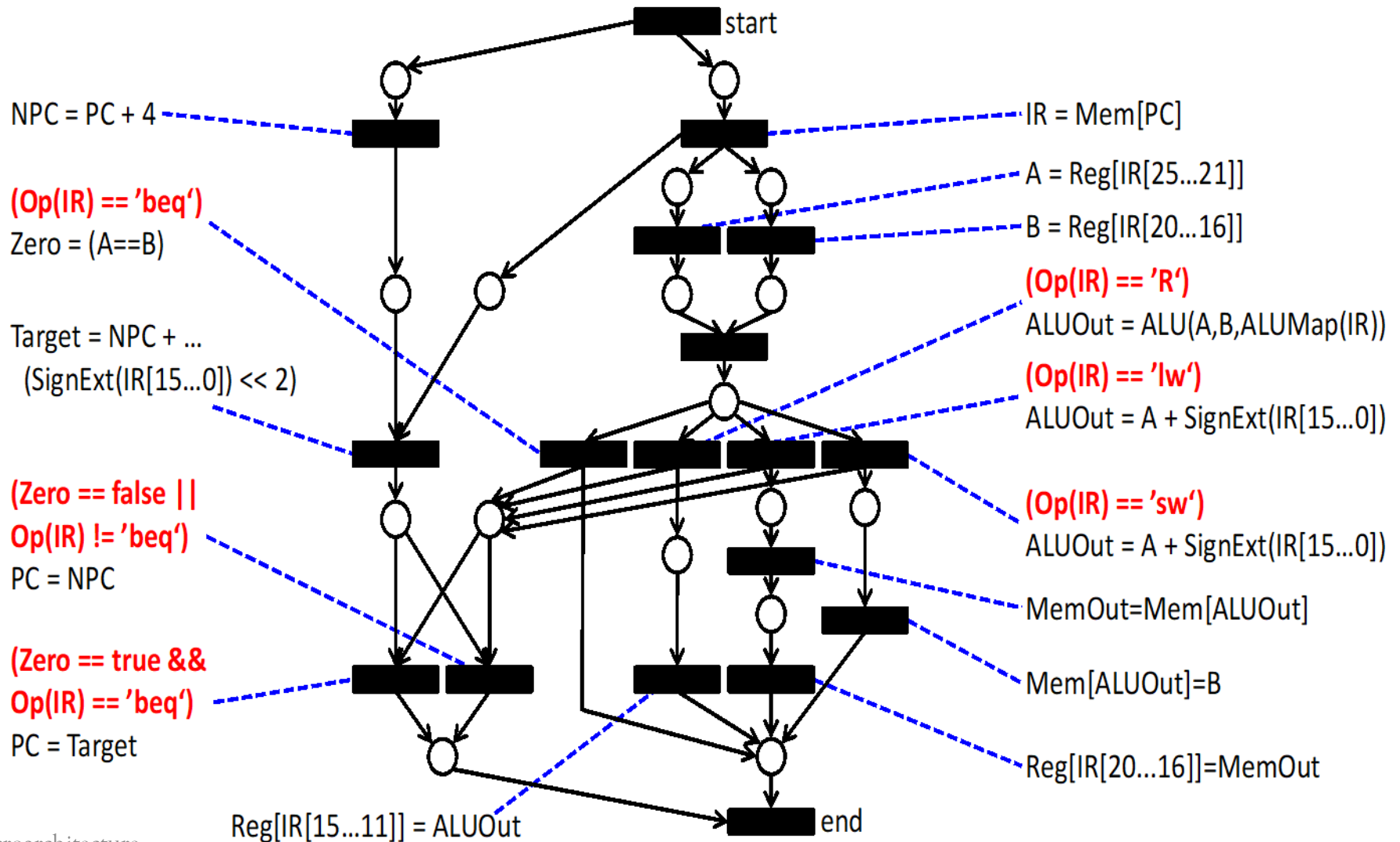
# MIPS refinement (without j instruction)




# High-level structure

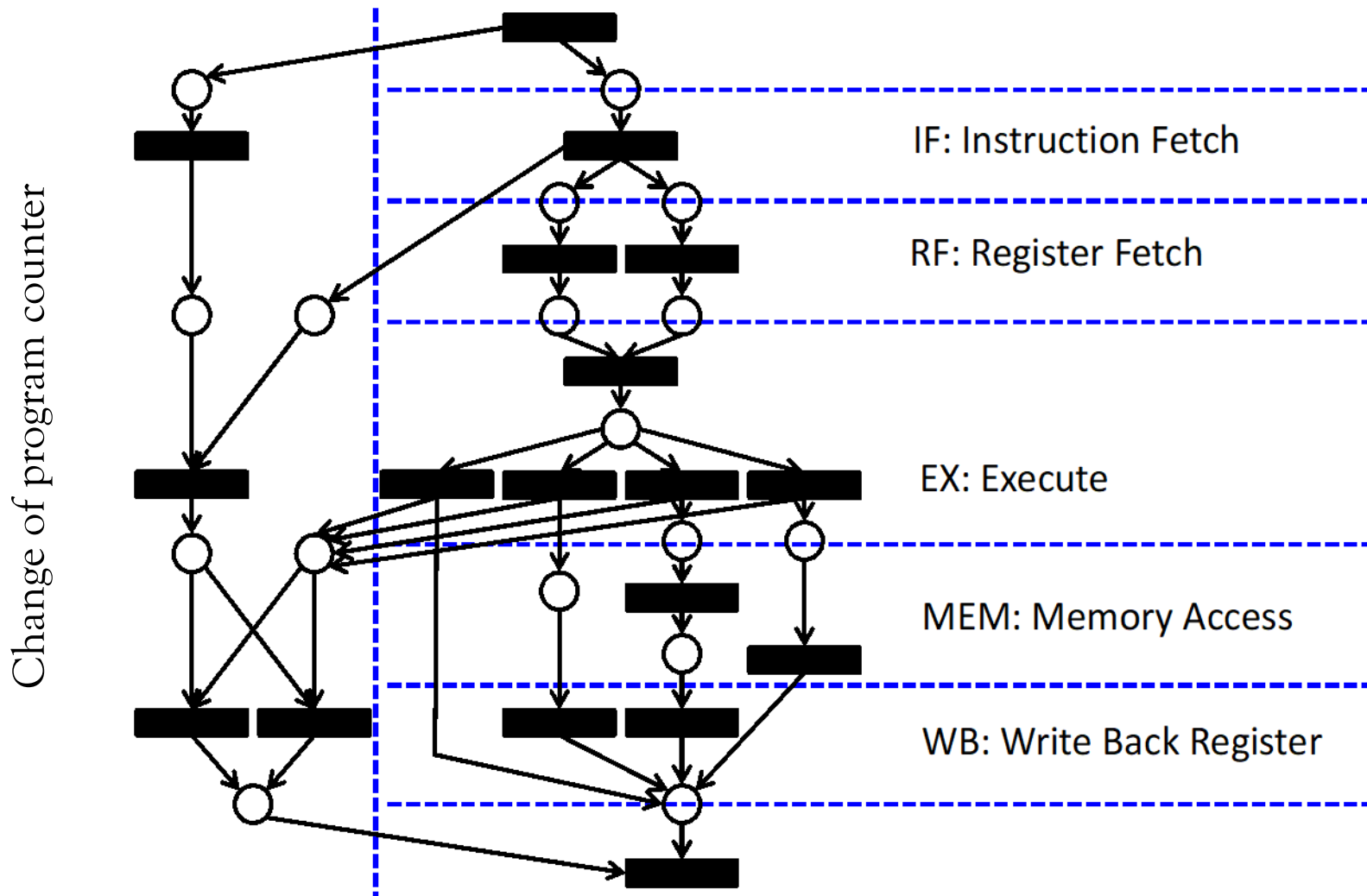
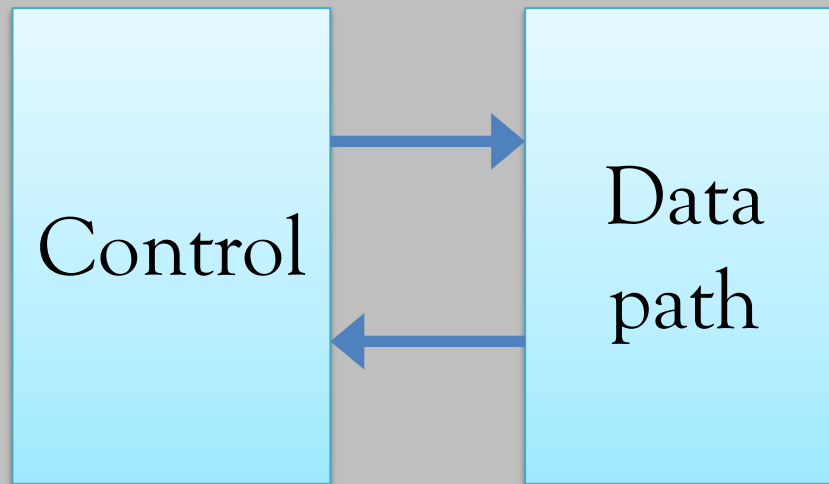
# Single-cycle implementation

All operations are executed in a single cycle.




Combinatorial circuit; implements the **structure** of the Petri net.

Implements all **operations** that are associated with the transitions of the Petri net.


# Synchronous sequential circuit design
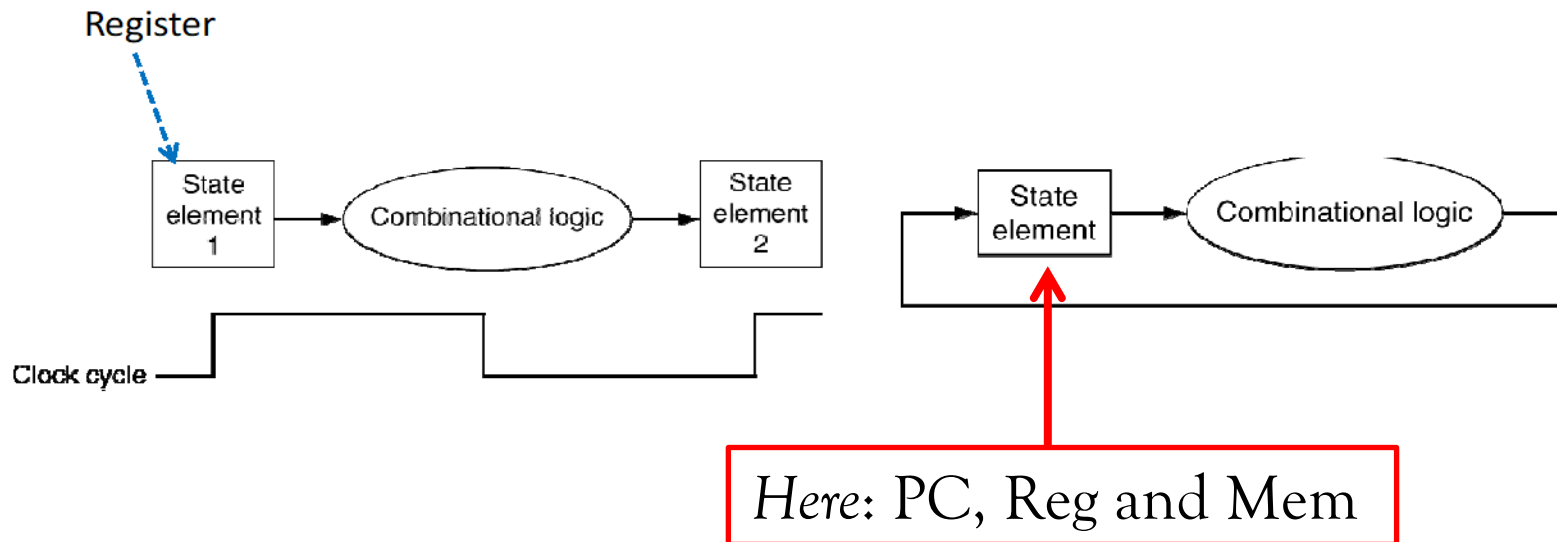
## Single-cycle system:

- Combinatorial logic processes data between the rising clock edges
- The *longest delay* between register outputs and register inputs determines the *minimal clock period*.
- Synchronous  $\rightarrow$  changes to memory elements are synchronized by a clock signal




# Memories in the MIPS datapath

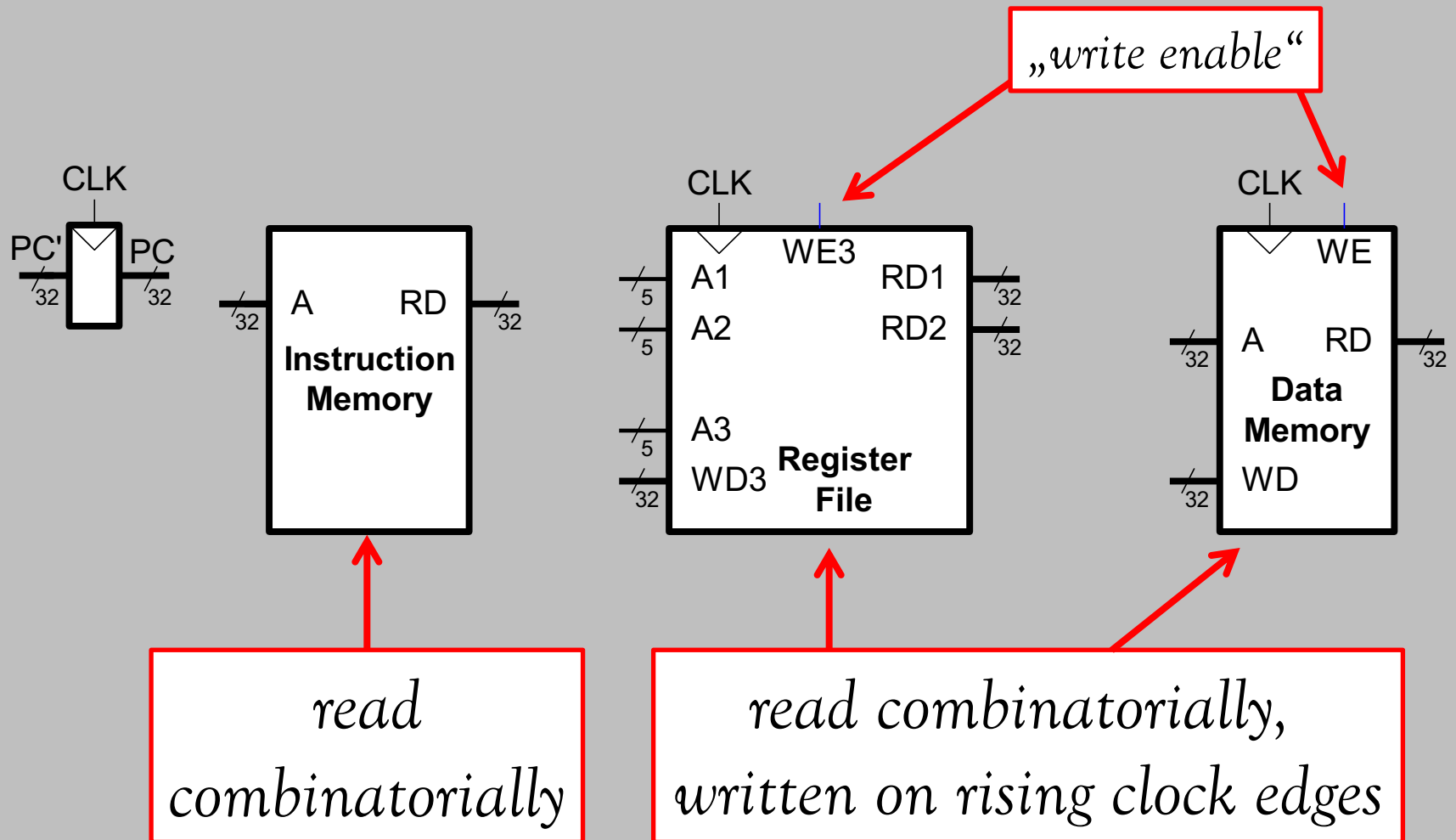


# Single-cycle datapath: lw instruction

- Step 1: „Instruction fetch“

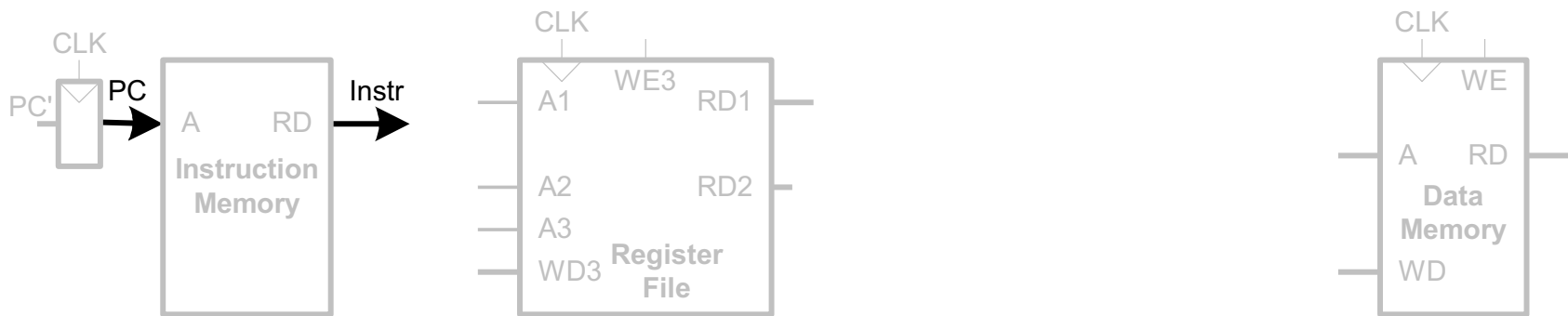

# Single-cycle datapath: lw instruction


- Step 2: „Register fetch“

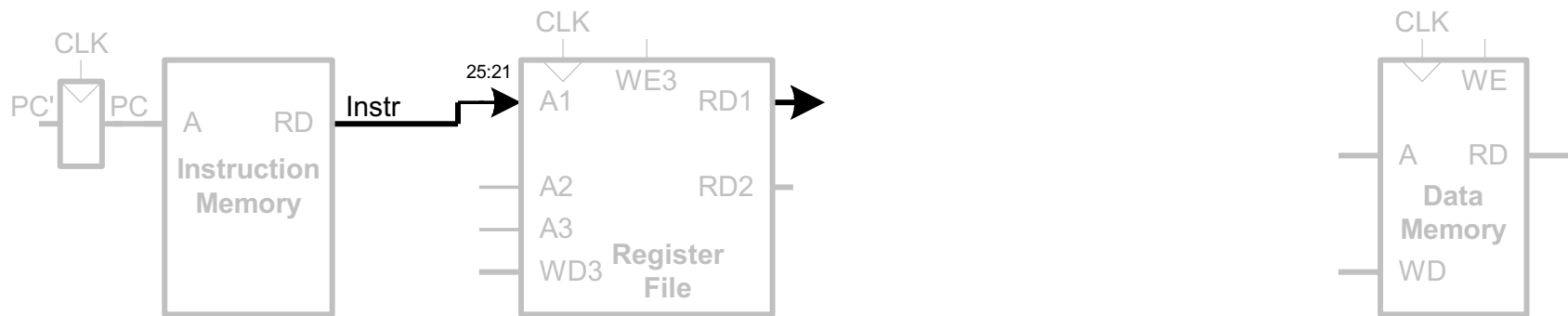




# Single-cycle datapath: lw instruction

- Step 3: Sign extension

 


# Single-cycle datapath: lw instruction

- Step 4: Compute memory address

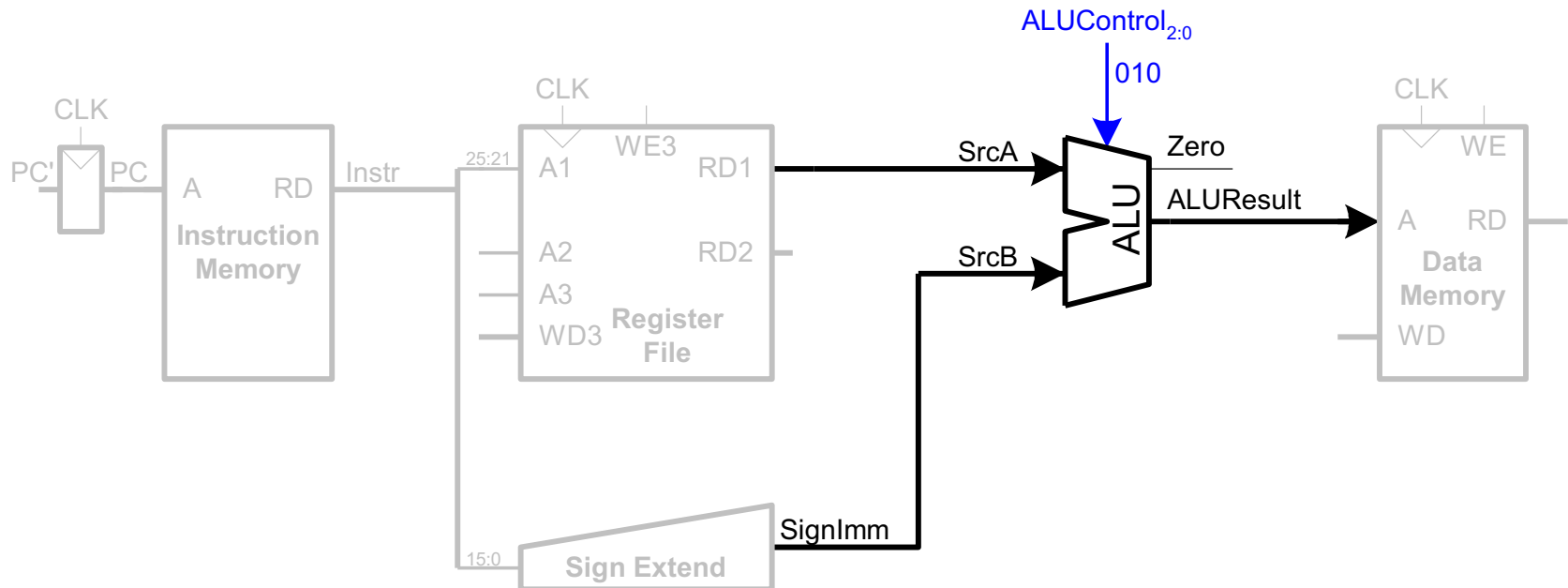

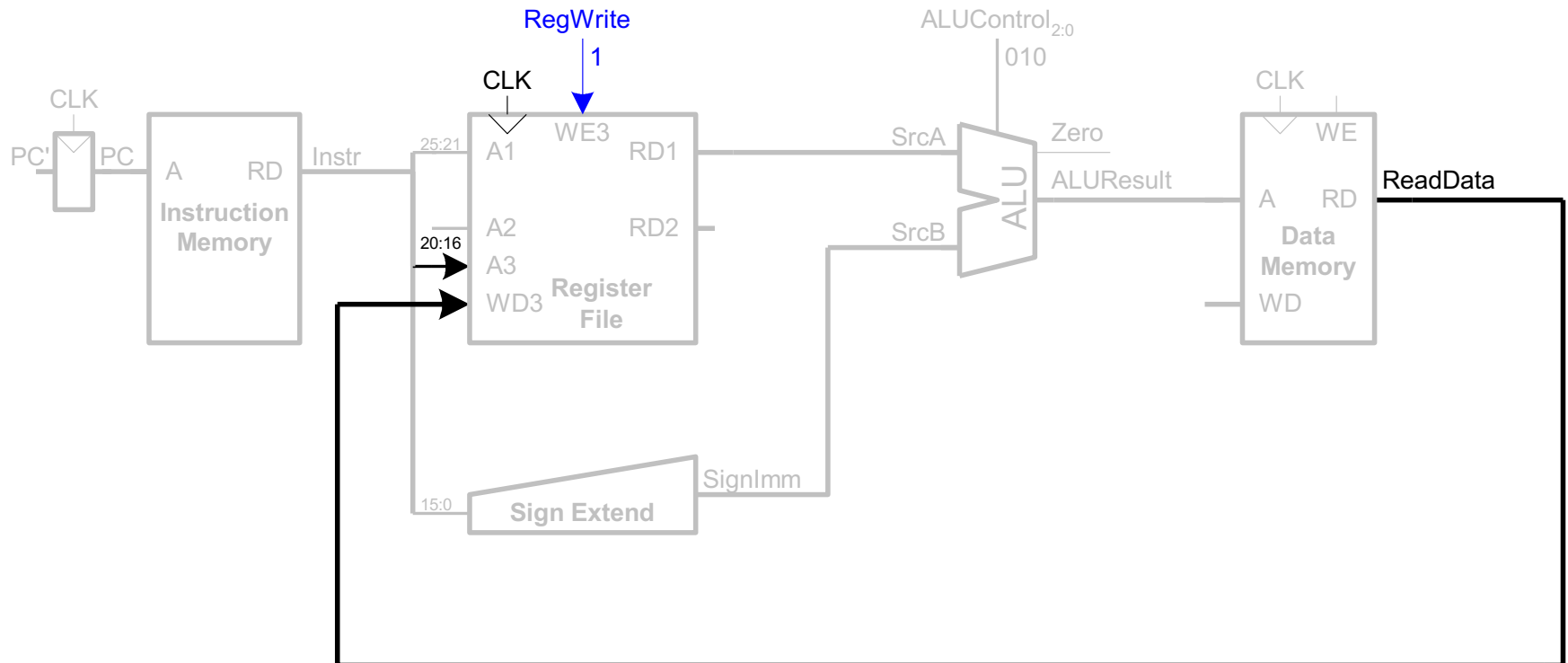
# Single-cycle datapath: lw instruction

- Step 5: Load data from memory and write it back into the register file



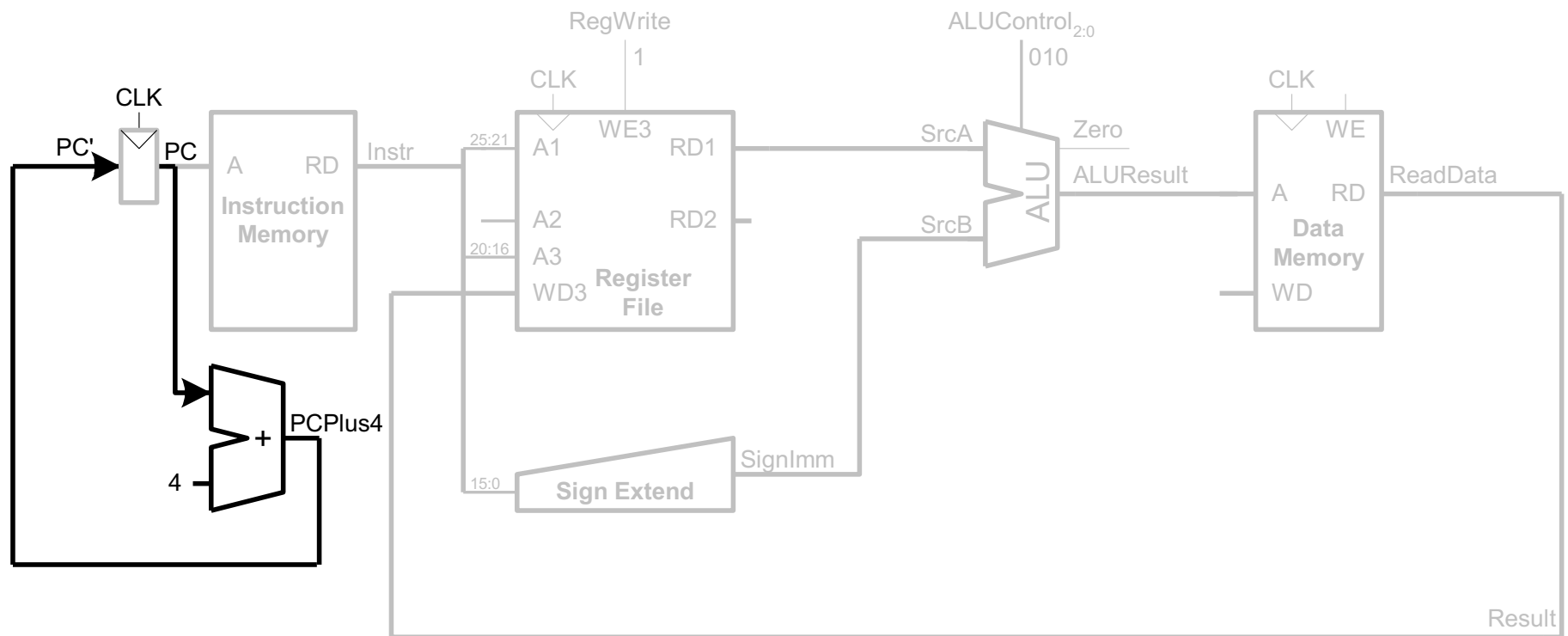
# Single-cycle datapath: lw instruction

- Step 6: Determine address of next instruction



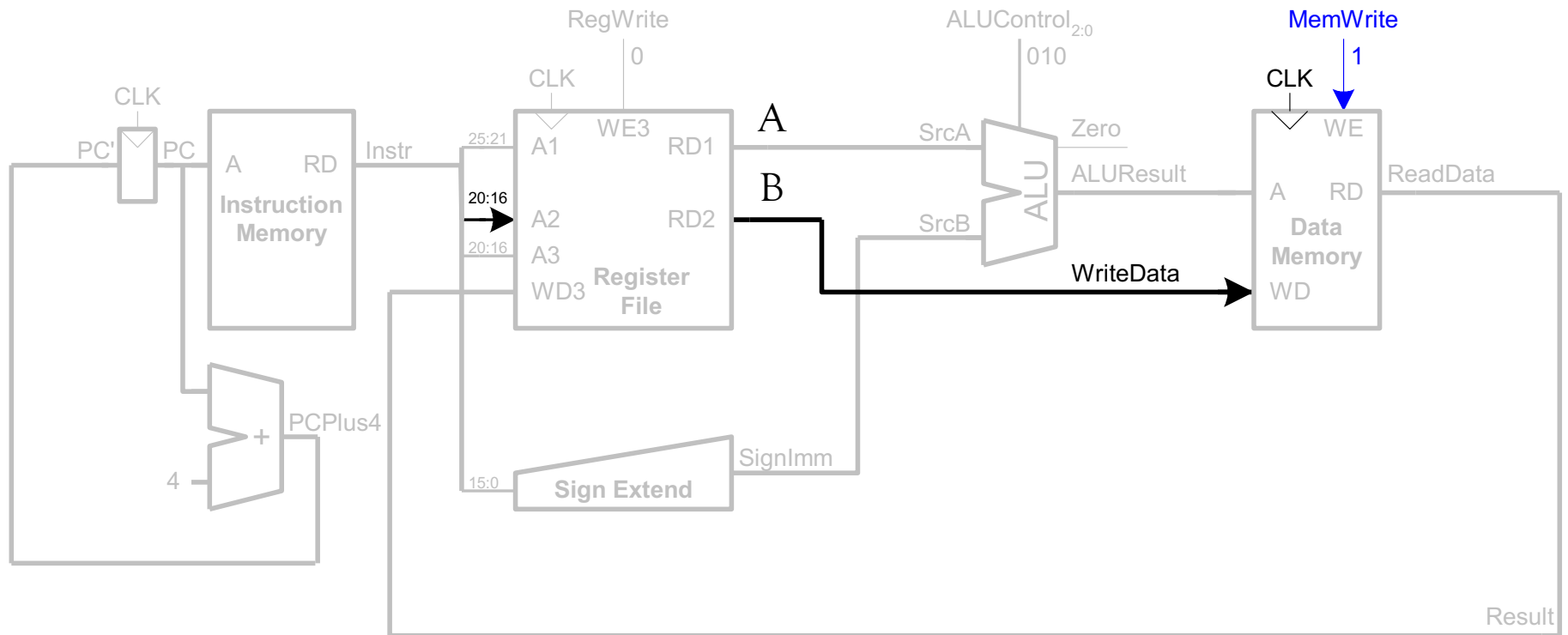
# Single-cycle datapath: sw instruction

- Store data from  $\text{Reg}[rt]$  into memory:



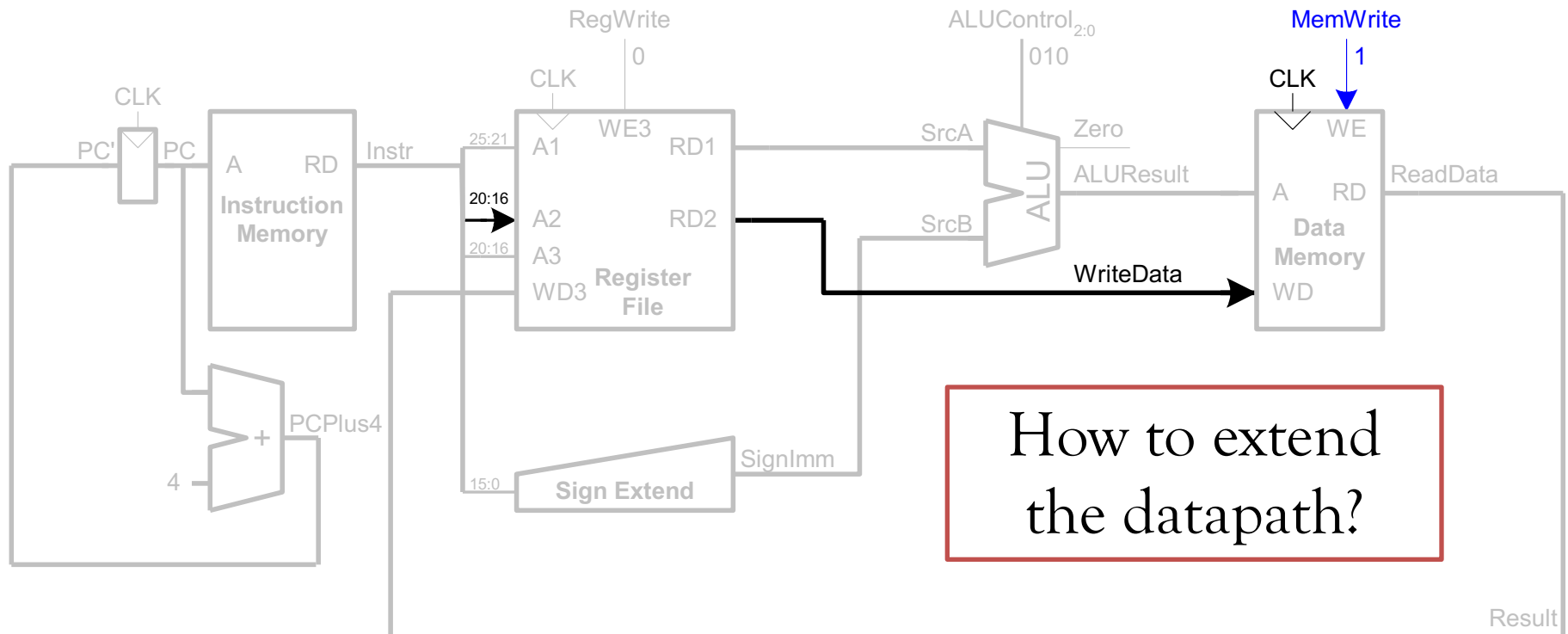
# Single-cycle datapath: R-type instructions

- Read operands from `rs` and `rt`
- Write `ALUResult` into register file
- Target register: `rd` (instead of `rt` in case of `load word`)


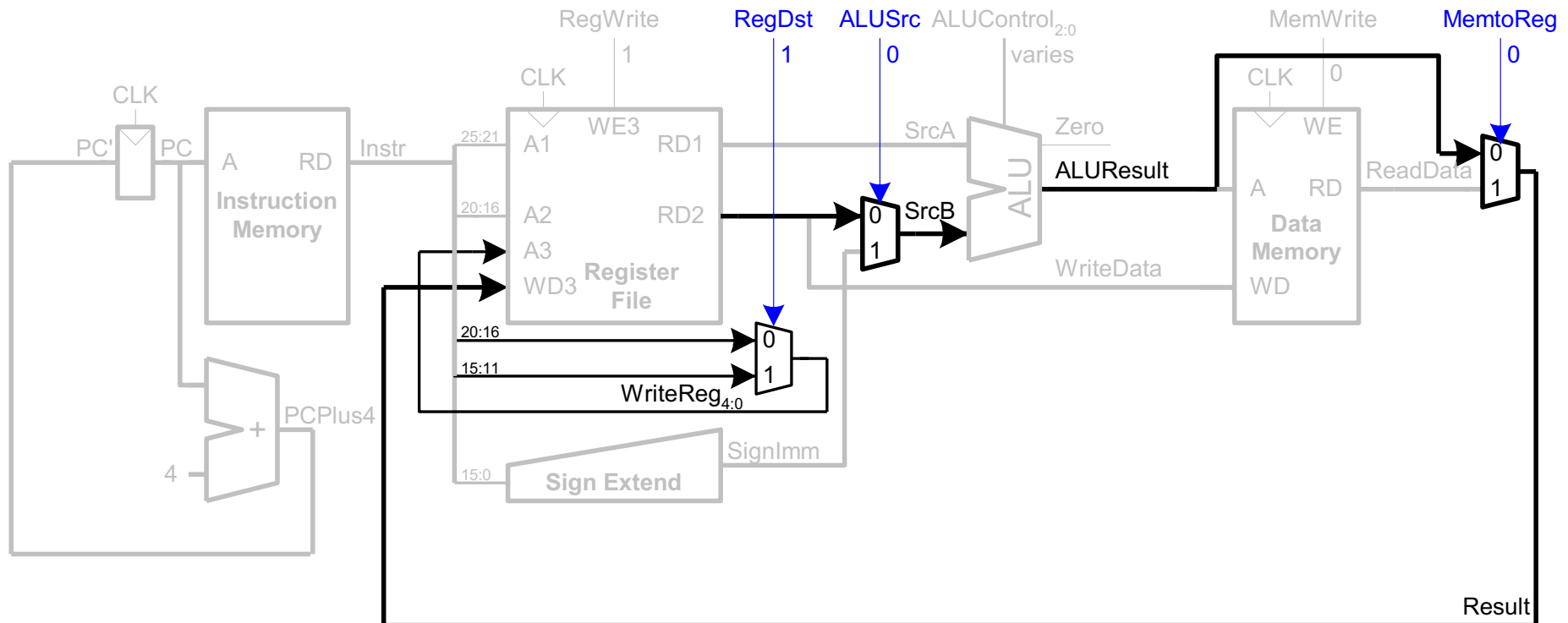
# Single-cycle datapath: R-type instructions

- Read operands from `rs` and `rt`
- Write `ALUResult` into register file
- Target register: `rd` (instead of `rt` in case of `load word`)




# Single-cycle datapath : beq instruction

- Determine whether  $rs$  is equal to  $rt$ .

- Compute branch target address:

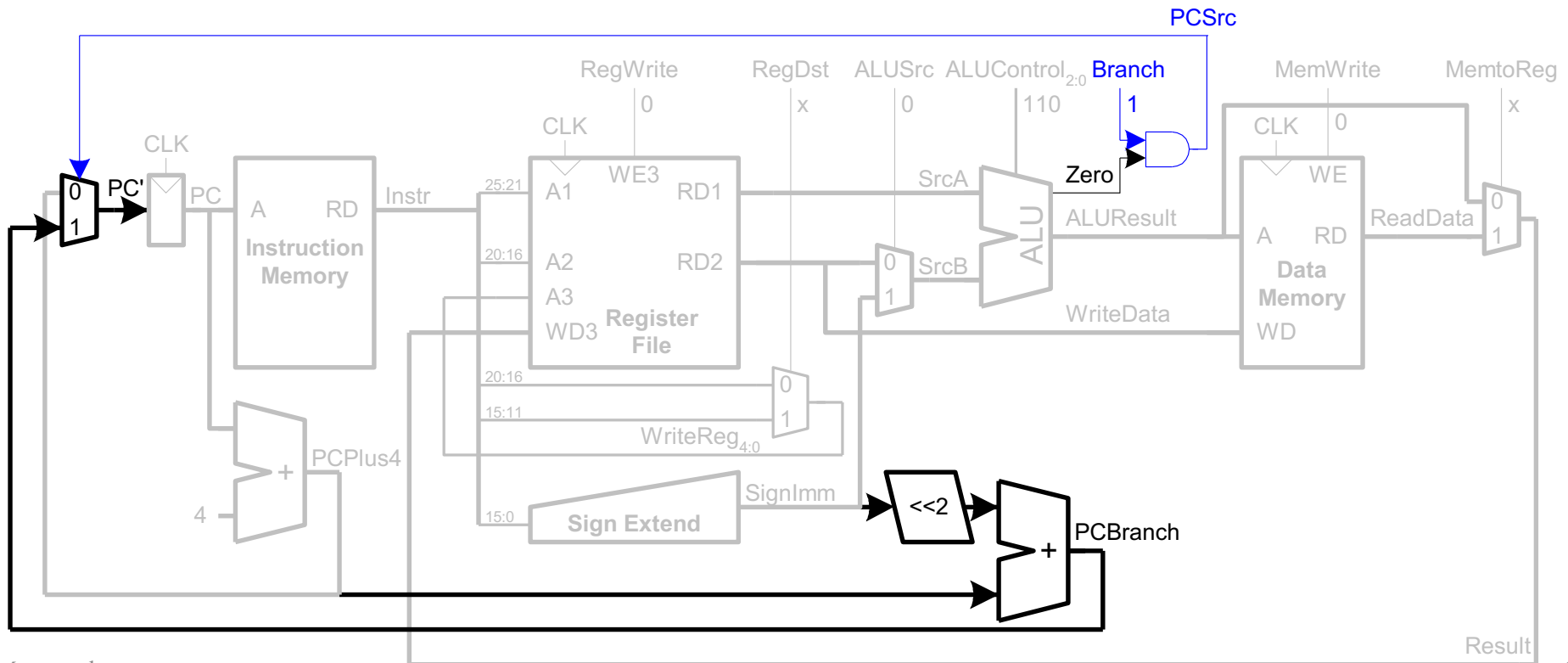
$$BTA = \text{SignExt}(IR[15..0]) \ll 2 + (PC + 4)$$






# Single-cycle processor


*Here: with combinatorial control*

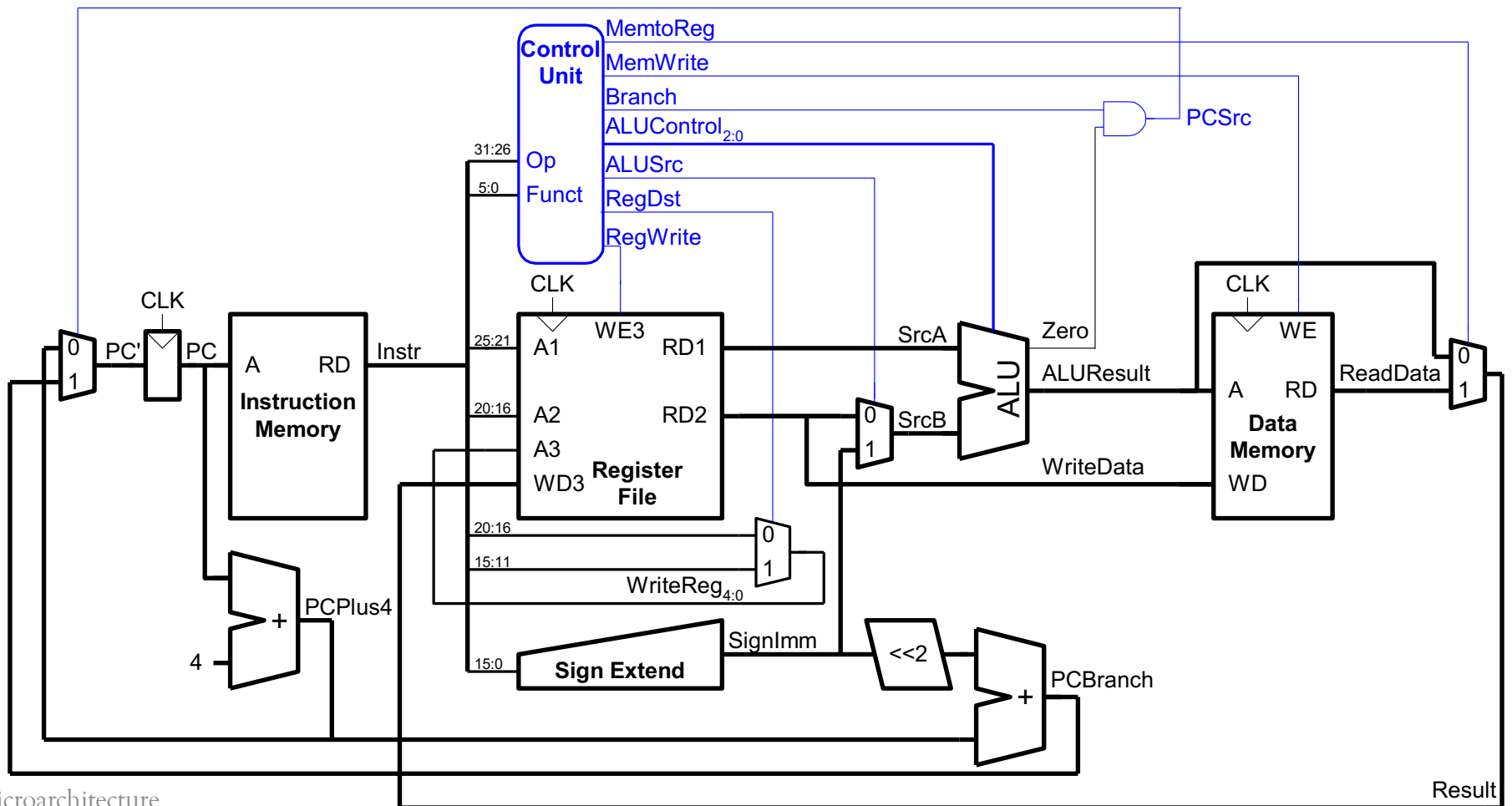

# Single-cycle control unit

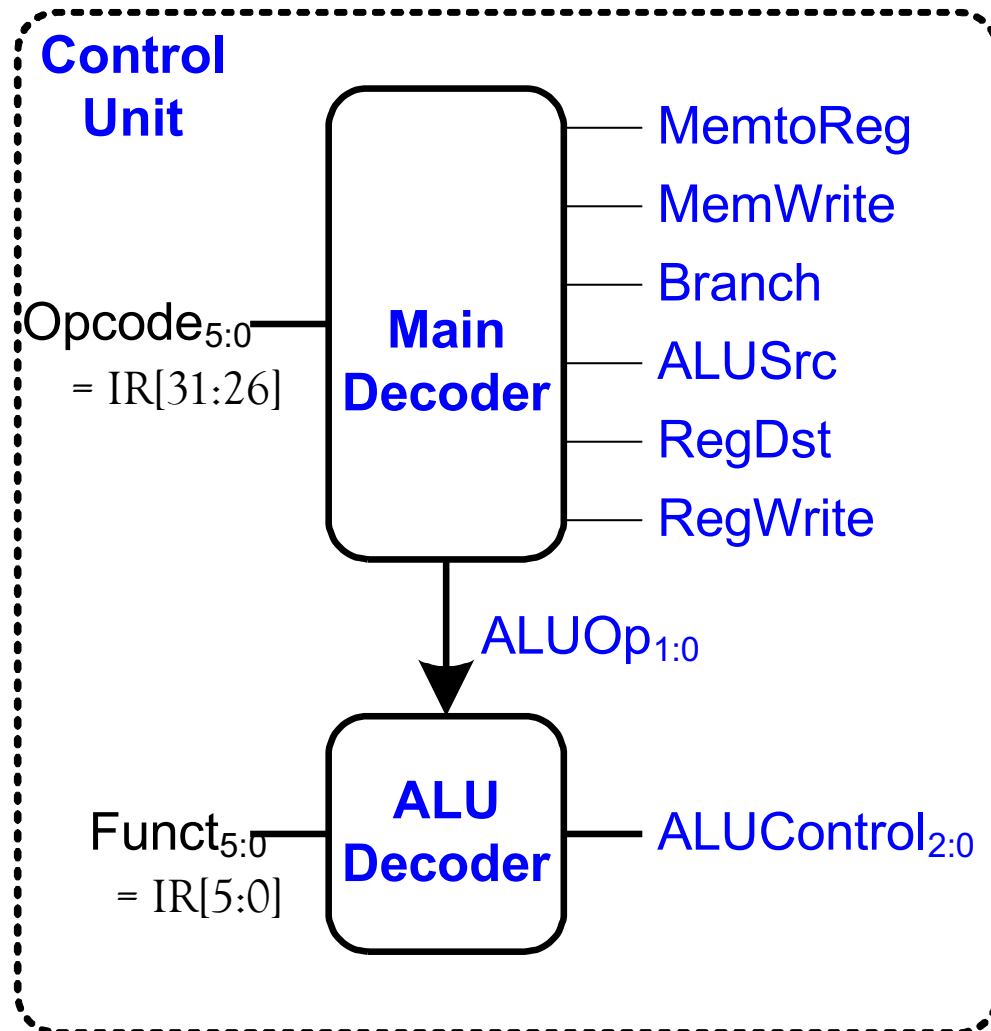


# Assumptions about the ALU

 

$F_{2:0}$	Function
000	A & B
001	A   B
010	A + B
011	not used
100	A & ~B
101	A   ~B
110	A - B
111	SLT

“set less than”

# ALU implementation

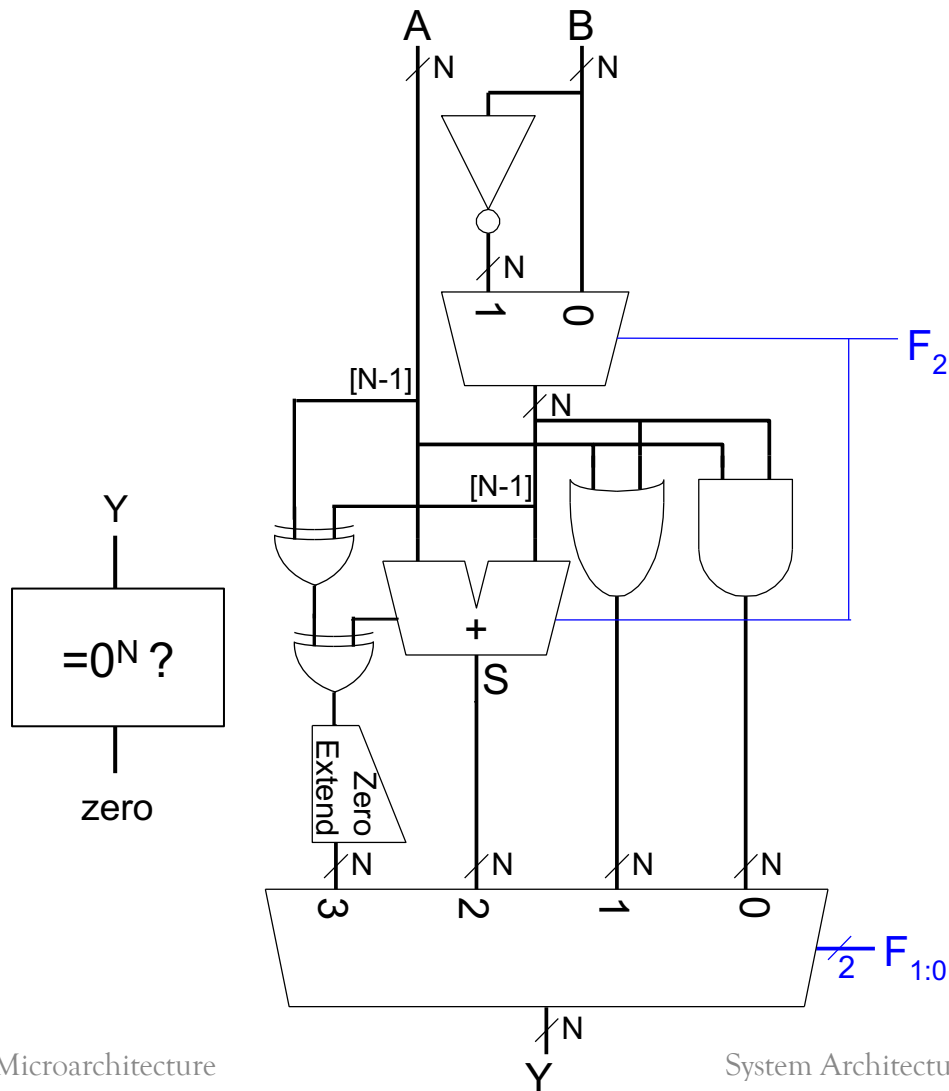

F <sub>2:0</sub>	Function
000	A & B
001	A   B
010	A + B
011	not used
100	A & ~B
101	A   ~B
110	A - B
111	SLT

# Control unit: ALU decoder


ALUOp <sub>1:0</sub>	Meaning
00	Add
01	Subtract
10	Look at Funct
11	Not Used

X = Don't Care

ALUOp <sub>1:0</sub>	Funct	ALUControl <sub>2:0</sub>
00	X	010 (Add)
01	X	110 (Subtract)
10	100000 (add)	010 (Add)
10	100010 (sub)	110 (Subtract)
10	100100 (and)	000 (And)
10	100101 (or)	001 (Or)
10	101010 (slt)	111 (SLT)
11	X	X

# Control unit: Main decoder


Instruction	Op <sub>5:0</sub>	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp <sub>1:0</sub>
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01

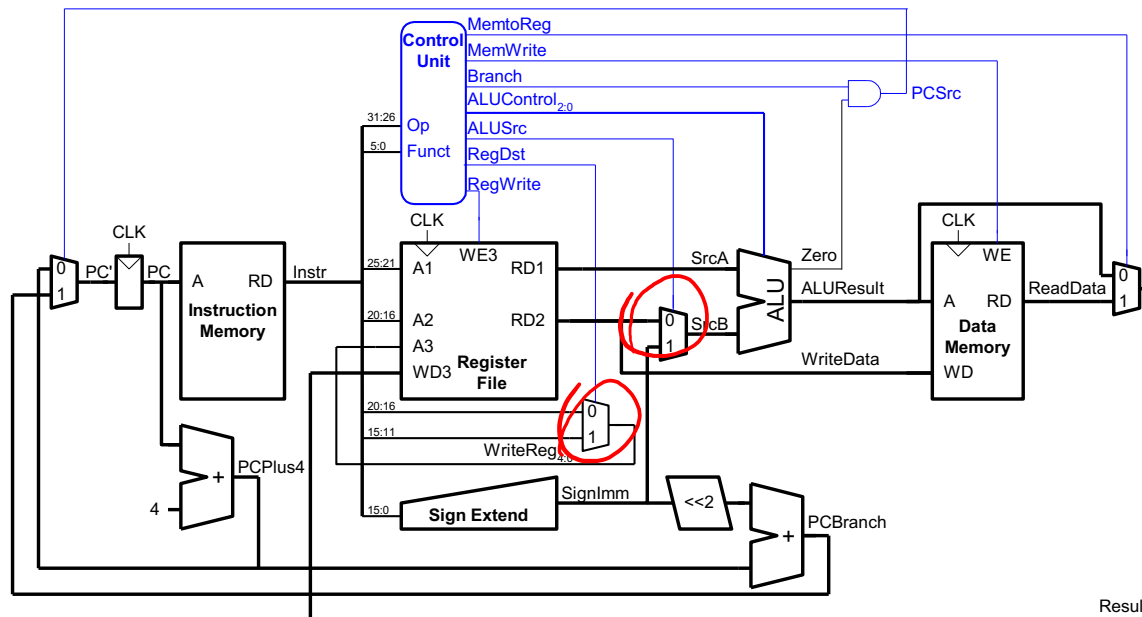

# Control unit: Main decoder


Instruction	Op <sub>5:0</sub>	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp <sub>1:0</sub>
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01

# Example: Single-cycle processor: or

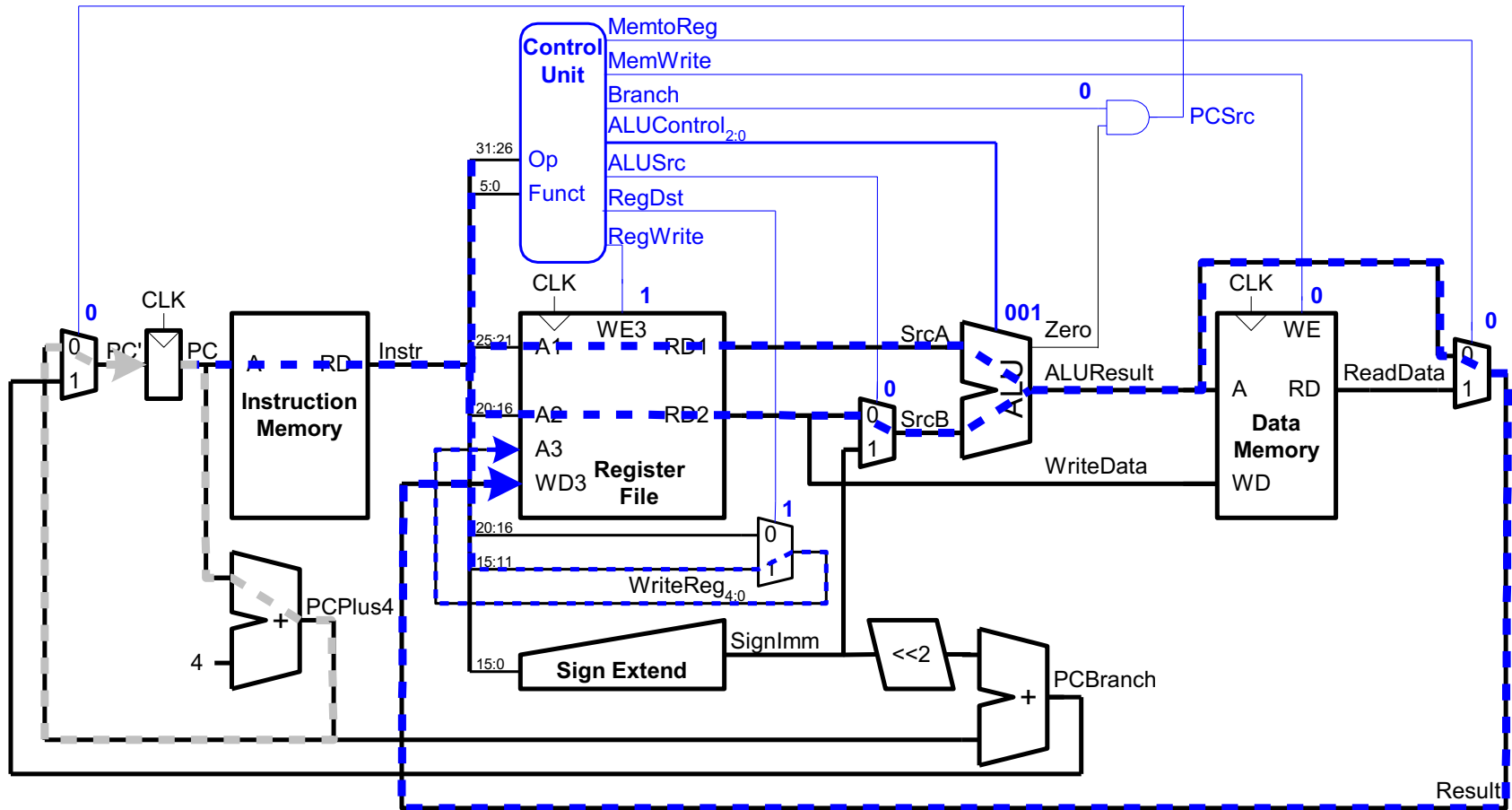



# Single-cycle datapath: Extension for j

 

# Control unit: Main decoder: Extension for j

Instruction	Op <sub>5:0</sub>	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp <sub>1:0</sub>	Jump
R-type	000000	1	1	0	0	0	0	10	0
lw	100011	1	0	1	0	0	1	00	0
sw	101011	0	X	1	0	1	X	00	0
beq	000100	0	X	0	1	0	X	01	0
<b>j</b>	<b>000010</b>	<b>0</b>	<b>X</b>	<b>X</b>	<b>X</b>	<b>0</b>	<b>X</b>	<b>XX</b>	<b>1</b>

# Conclusions

- **Petri nets** to describe the interpretation of MIPS instructions
  - **Datapath** corresponds to *components* that implement the transitions of the Petri net
  - **Control** derived from *structure* and *conditions* of the Petri net
- In the single-cycle processor the control is *combinatorial*